

# COMSM1302

## Overview of Computer Architecture

### Lecture 5

### Storage



# In this lecture

## Foundations

- Data representation, logic, Boolean algebra.

## Building blocks

- Transistors, transistor based logic, simple devices, **storage**.

## Modules

- Memory, simple controllers, FSMs, processors and execution.

## Programming

- Machine code, assembly, high-level languages, compilers.

## Wrap-up

- Operating systems, energy aware computing.



# Previous lecture

- We can do **basic arithmetic** with a **bunch of NAND gates**!

Imagine if we could **store** the results of that arithmetic.

**Today we learn how.**



# Combinatorial vs. sequential logic


- So far, everything we have done is **combinatorial** logic.
  - Input signals are combined in various ways to produce output signals.
  - By **connecting blocks together** we can build more complex circuits.
- If we **change inputs**, the **outputs change** shortly afterwards.
  - Signals take some (very small) time to propagate.



# 🔥 Ring Oscillator




What does the below device do?

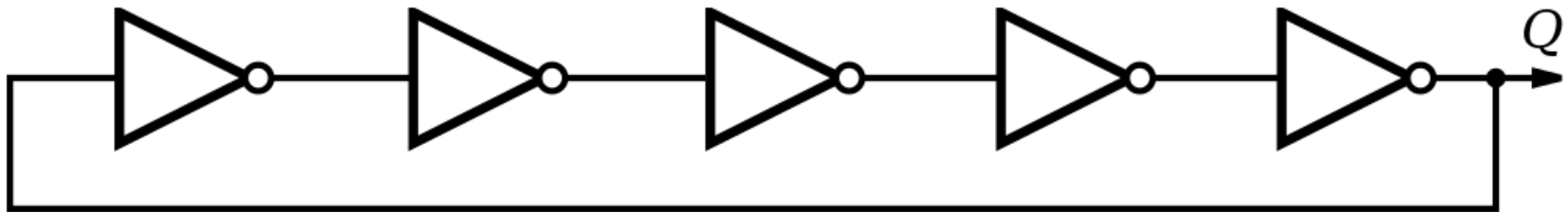

# 🔥 Ring Oscillator

What does the below device do?

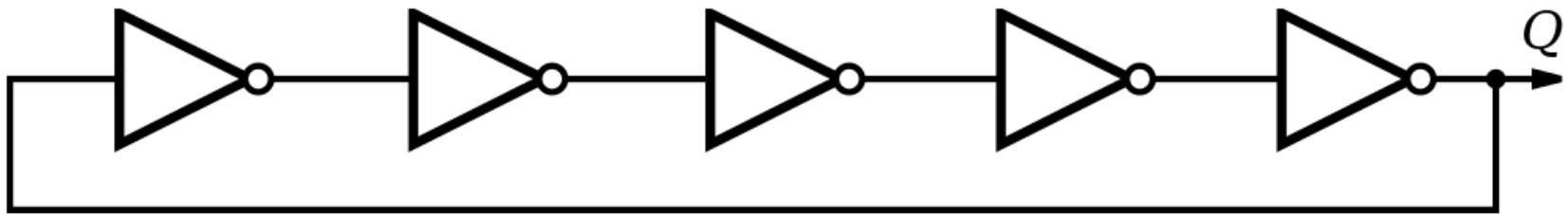

A **ring oscillator** is a device composed of an **odd number of NOT gates** in a **ring**. The output oscillates between two voltage levels, representing true and false. The NOT gates, or inverters, in a ring oscillator are **connected in a chain** and the output of the last inverter is fed back into the first, forming a circular chain, or a ring.


*Can a circular chain composed of an even number of inverters be used as a ring oscillator?*

# Ring Oscillator

- The output oscillates between 1 and 0.
- How fast?

$$F_{osc} = \frac{1}{N \times 2D_{inv}}$$

- $N$  is the **number of inverters**.

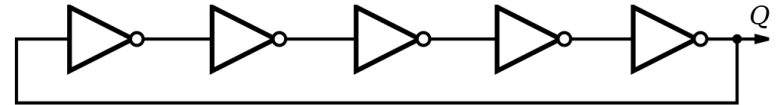

- $D_{inv}$  – the **inverter delay**, is determined by:
  - Wire length
  - Device size
  - Voltage
  - Temperature
  - Material
  - ...



# Combinatorial vs. sequential logic

- What if we wanted to perform the following arithmetic:

$$Y = 24 + 15 + 100$$

- But we can only add two numbers together at a time.
- We can create a sequence:

$$X = 24 + 15$$

$$Y = X + 100$$

- We want to take the **output** of our **first addition** and make it one of the **inputs** to our **second addition**.

**It's not *quite* that simple.**






# 🔥 Combinatorial vs. sequential logic

- To enforce a sequence reliably, we can:
  - Store result values
  - Control when values are stored
- This allows us to build a *sequential* system, combining **storage** and **combinatorial logic**.

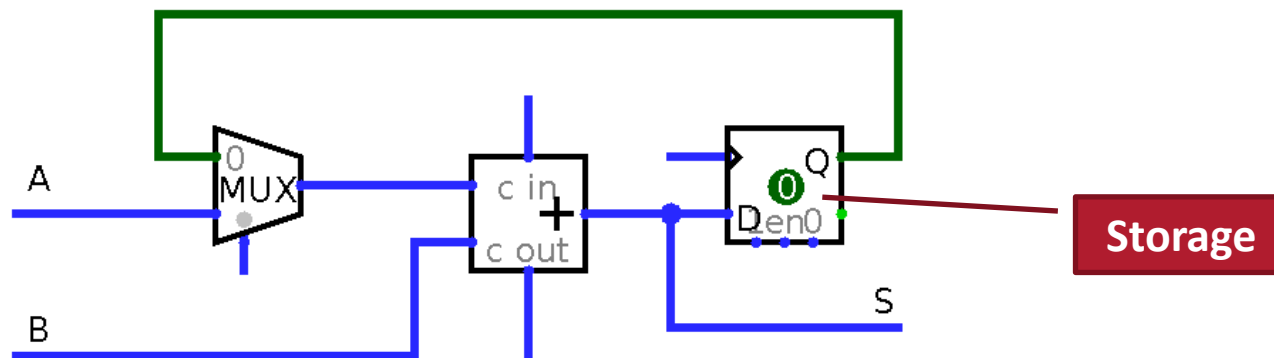
**Below: A *prototype* we'll explain, develop and complete!**


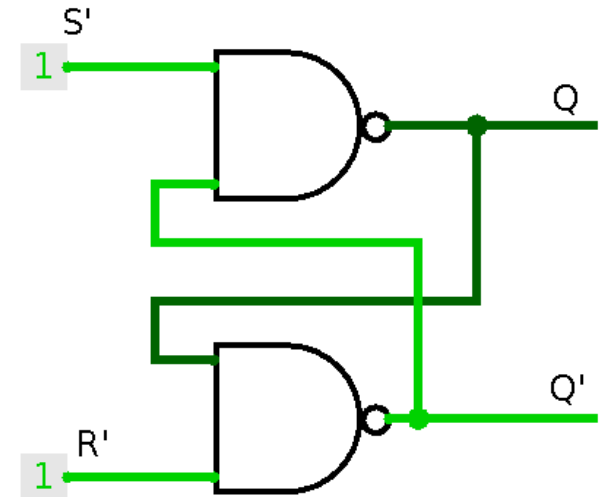
# SR-latch



- Two NAND gates
- Input signals are **active-low**.
  - Denoted with top bar or tick, e.g.  $\overline{S}$  or  $S'$
  - active high/low tells you what logic value is necessary for you to activate an input
    - **active high** is active when set to 1
    - **active low** is active when set to 0
- Start from  $S' = R' = 1$



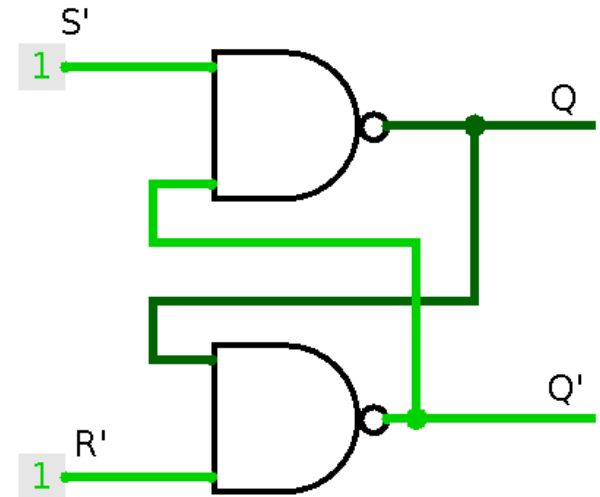
# SR-latch



$\mu$

- Two NAND gates
- Input signals are **active-low**.
  - Denoted with top bar or tick, e.g.  $\overline{S}$  or  $S'$
  - active high/low tells you what logic value is necessary for you to activate an input
    - **active high** is active when set to 1
    - **active low** is active when set to 0
- Start from  $S' = R' = 1$



 
# SR-latch



$\mu$

- Two NAND gates
- Input signals are **active-low**.
  - Denoted with top bar or tick, e.g.  $\overline{S}$  or  $S'$
  - active high/low tells you what logic value is necessary for you to activate an input
    - **active high** is active when set to 1
    - **active low** is active when set to 0
- Start from  $S' = R' = 1$
- **Set the latch**
  - $S' = 0$



A	B	A NAND B
1	1	0
1	0	1
0	1	1
0	0	1



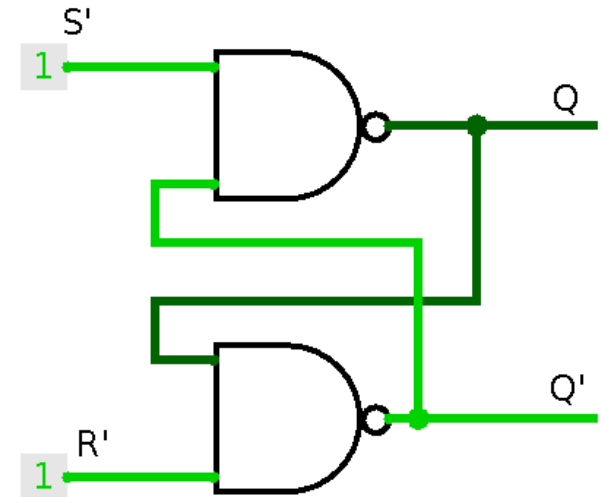
# SR-latch



$\mu$


- Two NAND gates
- Input signals are **active-low**.
  - Denoted with top bar or tick, e.g.  $\overline{S}$  or  $S'$
  - active high/low tells you what logic value is necessary for you to activate an input
    - **active high** is active when set to 1
    - **active low** is active when set to 0
- Start from  $S' = R' = 1$
- **Set the latch**
  - $S' = 0$




A	B	A NAND B
1	1	0
1	0	1
0	1	1
0	0	1



# SR-latch

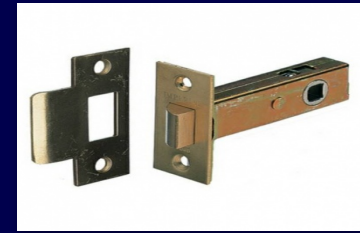

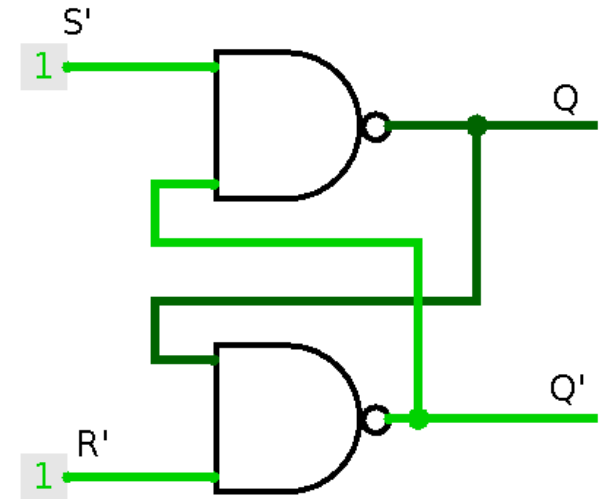- Two NAND gates
- Input signals are **active-low**.
  - Denoted with top bar or tick, e.g.  $\overline{S}$  or  $S'$
  - active high/low tells you what logic value is necessary for you to activate an input
    - **active high** is active when set to 1
    - **active low** is active when set to 0
- Start from  $S' = R' = 1$
- **Set the latch**
  - $S' = 0$
- **Reset the latch**
  - $R' = 0$




A	B	A NAND B
1	1	0
1	0	1
0	1	1
0	0	1



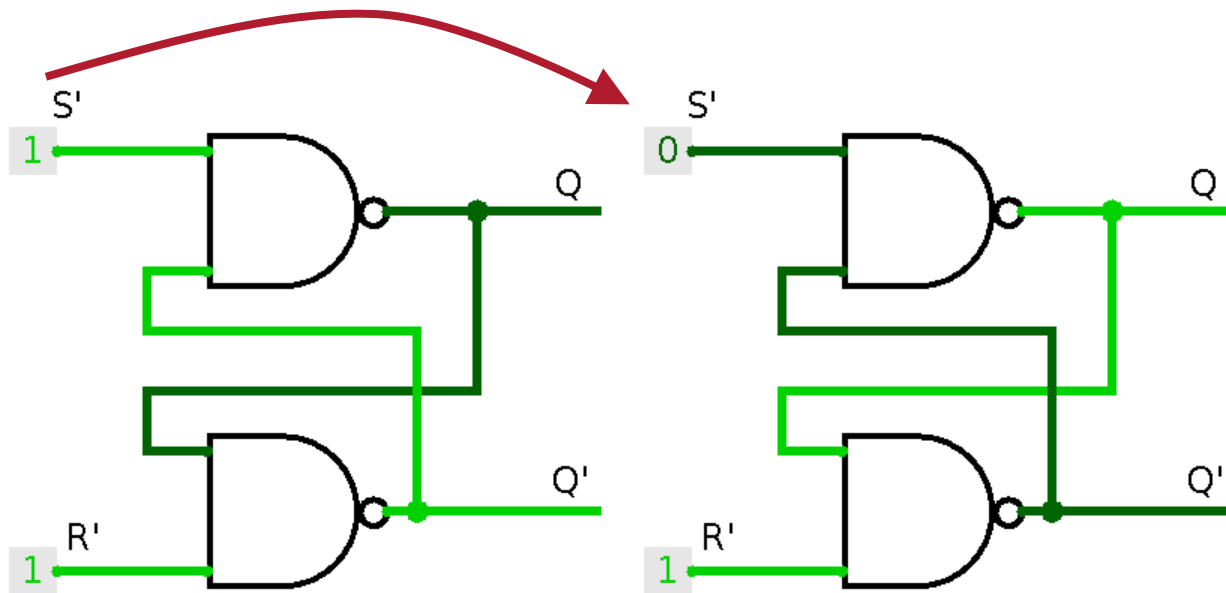
# 🔥 Setting the latch

- When  $S'$  transitions to low,  $Q$  is **set high** (and  $Q'$  its inverse).


 
# 🔥 Setting the latch


- When  $S'$  transitions to low,  $Q$  is **set high** (and  $Q'$  its inverse).
- Upon  $S'$  returning to high...  $Q$  retains the same high value.





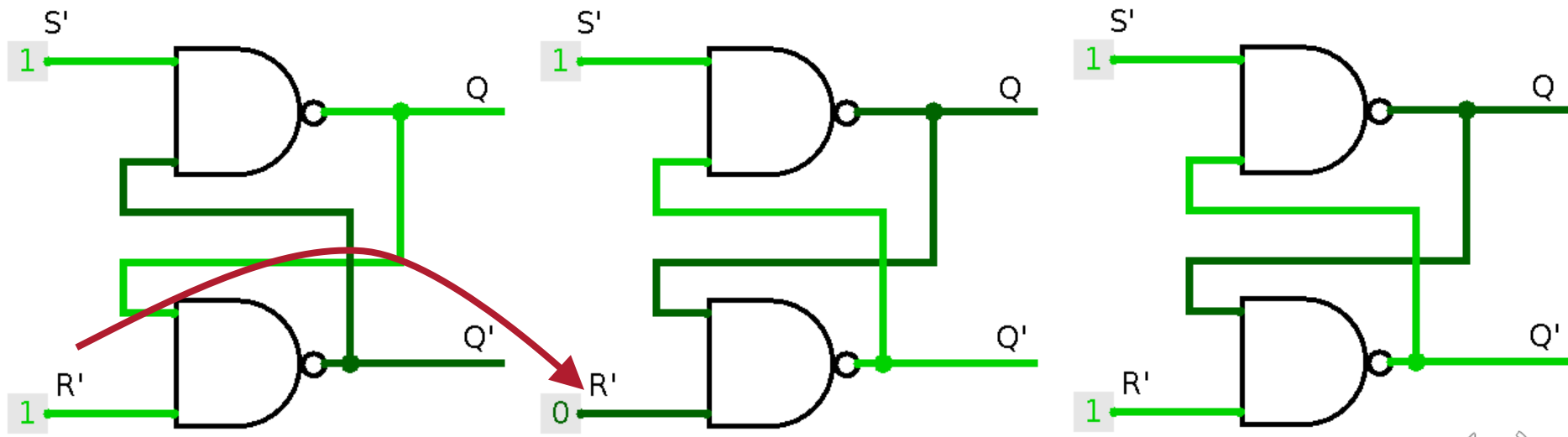
# 🔥 Resetting the latch

- When  $R'$  transitions to low,  $Q$  is **reset low**.


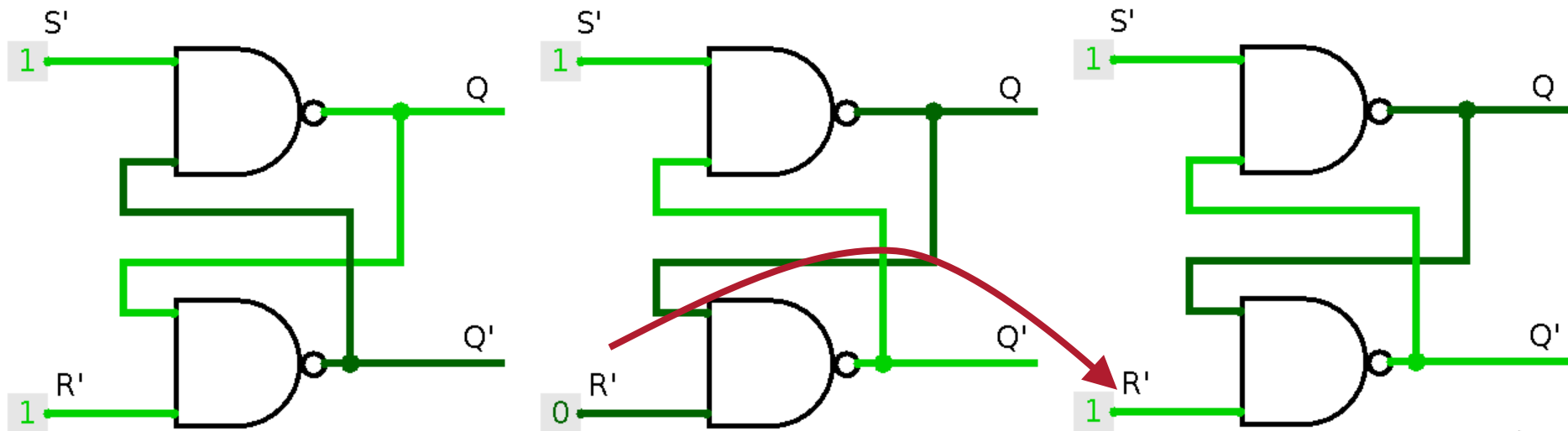
# 🔥 Resetting the latch

- When  $R'$  transitions to low,  $Q$  is **reset low**.
- Upon  $R'$  returning to high...  $Q$  retains the same low value.




# SR inputs

A	B	A NAND B
1	1	0
1	0	1
0	1	1
0	0	1

$S'$	$R'$	Q
1	1	Hold
1	0	0
0	1	1
0	0	

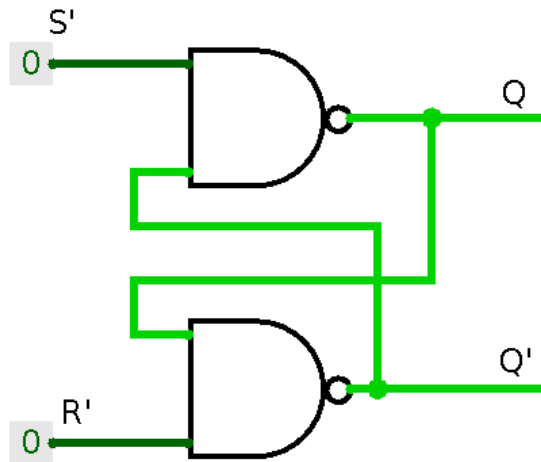
- There are **three valid** combinations of  $S'$  and  $R'$  for the SR NAND latch.



# SR inputs

A	B	A NAND B
1	1	0
1	0	1
0	1	1
0	0	1

$S'$	$R'$	Q
1	1	Hold
1	0	0
0	1	1
0	0	Not allowed

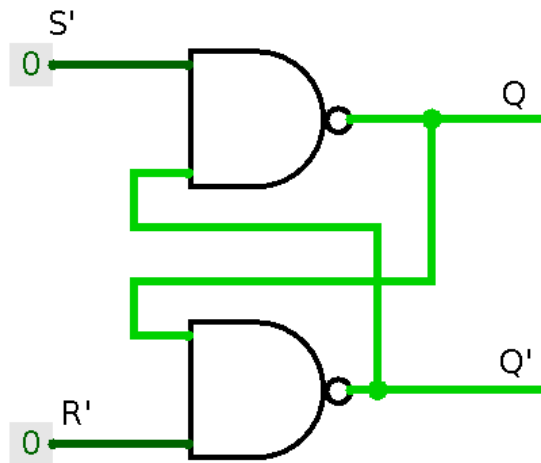


- There are **three valid** combinations of  $S'$  and  $R'$  for the SR NAND latch.
- Both  $S'$  and  $R'$  should **not be active** (low) together.

# SR inputs

A	B	A NAND B
1	1	0
1	0	1
0	1	1
0	0	1

S'	R'	Q
1	1	Hold
1	0	0
0	1	1
0	0	Not allowed

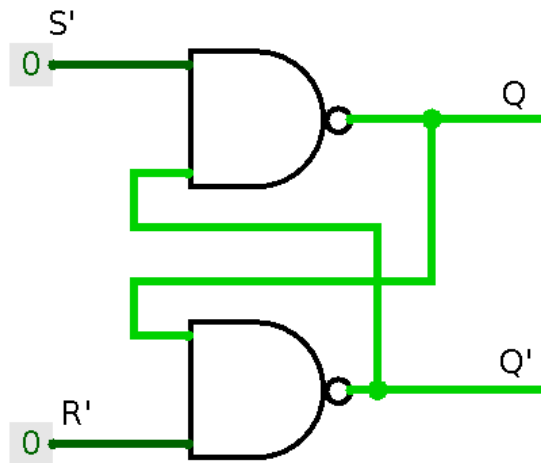

- There are **three valid** combinations of S' and R' for the SR NAND latch.
- Both S' and R' should **not be active** (low) together.

Why?




# SR inputs

A	B	A NAND B
1	1	0
1	0	1
0	1	1
0	0	1

S'	R'	Q	Q'
1	1	Q_prev	Q'_prev
1	0	0	1
0	1	1	0
0	0		

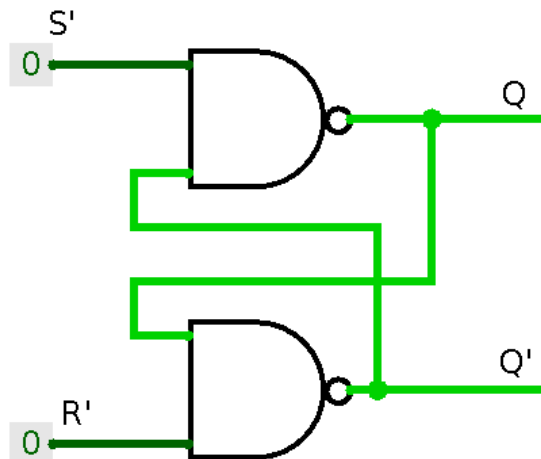- If both S' and R' were active at the same time, then the output ...




# SR inputs

A	B	A NAND B
1	1	0
1	0	1
0	1	1
0	0	1

S'	R'	Q	Q'
1	1	Q_prev	Q'_prev
1	0	0	1
0	1	1	0
0	0		

- If both S' and R' were active at the same time, then the output **would not make any sense**.

$$S' = 0, R' = 0, Q = Q'$$

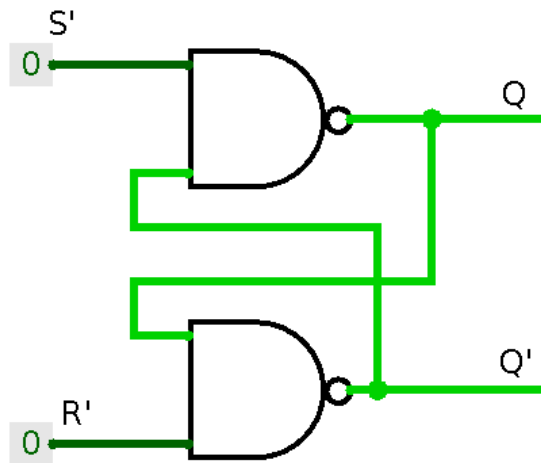


# 🔥 SR inputs

A	B	A NAND B
1	1	0
1	0	1
0	1	1
0	0	1

S'	R'	Q	Q'
1	1	Q_prev	Q'_prev
1	0	0	1
0	1	1	0
0	0	1	1

- If both S' and R' were active at the same time, then the output **would not make any sense.**

$$S' = 0, R' = 0, Q = Q'$$

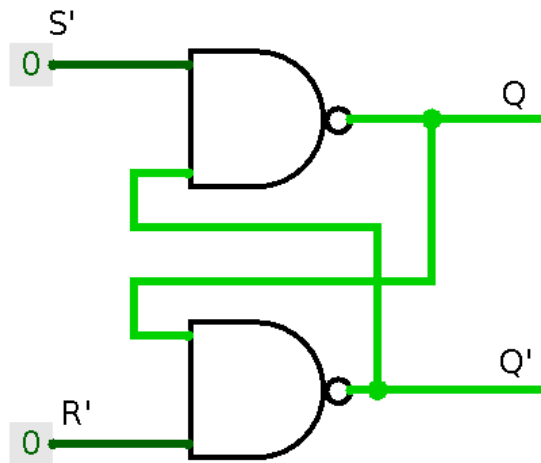




# 🔥 SR inputs

A	B	A NAND B
1	1	0
1	0	1
0	1	1
0	0	1

S'	R'	Q	Q'
1	1	Q_prev	Q'_prev
1	0	0	1
0	1	1	0
0	0	not allowed	

- If both S' and R' were active at the same time, then the output **would not make any sense.**


$$S' = 0, R' = 0, Q = Q'$$

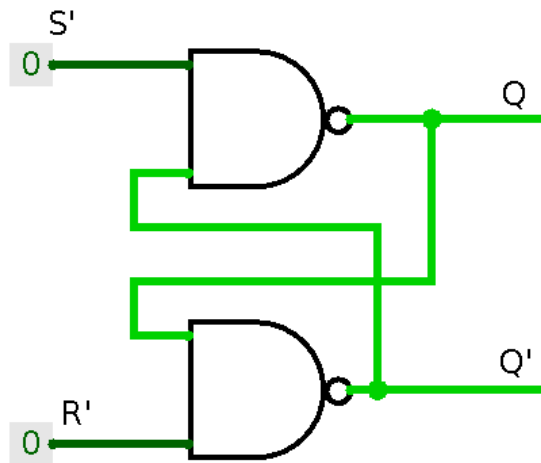

# 🔥 Different latch types

- We have seen an SR (Set-Reset) latch using NAND.
  - An SR latch can also be built from NOR gates.

How does this work?

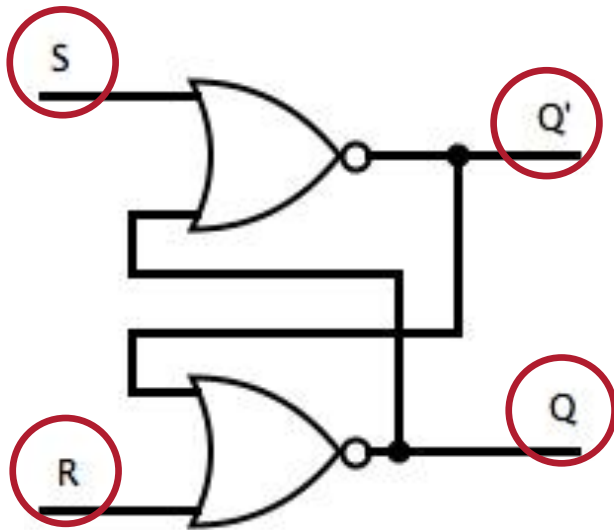


# 🔥 SR latch with NOR gates

A	B	A NOR B
1	1	0
1	0	0
0	1	0
0	0	1

- We have seen an SR (Set-Reset) latch using NAND.
  - An SR latch can also be built from NOR gates.

How does this work?

 


S	R	Q	Q_next	Q'_next
0	0	0		

# 🔥 SR latch with NOR gates

A	B	A NOR B
1	1	0
1	0	0
0	1	0
0	0	1

- We have seen an SR (Set-Reset) latch using NAND.
  - An SR latch can also be built from NOR gates.

How does this work?

 


S	R	Q	Q_next	Q'_next
0	0	0	0	1

# 🔥 SR latch with NOR gates

A	B	A NOR B
1	1	0
1	0	0
0	1	0
0	0	1

- We have seen an SR (Set-Reset) latch using NAND.
  - An SR latch can also be built from NOR gates.

How does this work?

 


S	R	Q	Q_next	Q'_next
0	0	0	0	1
1	0	0		

# 🔥 SR latch with NOR gates

A	B	A NOR B
1	1	0
1	0	0
0	1	0
0	0	1

- We have seen an SR (Set-Reset) latch using NAND.
  - An SR latch can also be built from NOR gates.

How does this work?

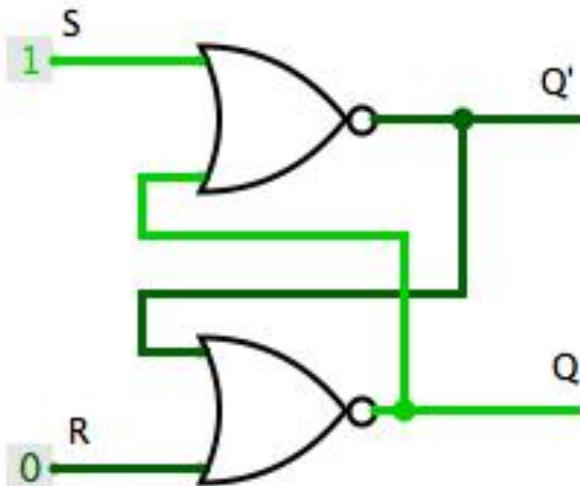


S	R	Q	Q_next	Q'_next
0	0	0	0	1
1	0	0	1	0

# 🔥 SR latch with NOR gates

A	B	A NOR B
1	1	0
1	0	0
0	1	0
0	0	1

- We have seen an SR (Set-Reset) latch using NAND.
  - An SR latch can also be built from NOR gates.

How does this work?

 


S	R	Q	Q_next	Q'_next
0	0	0	0	1
1	0	0	1	0
0	0	1		

# 🔥 SR latch with NOR gates

A	B	A NOR B
1	1	0
1	0	0
0	1	0
0	0	1

- We have seen an SR (Set-Reset) latch using NAND.
  - An SR latch can also be built from NOR gates.

How does this work?

 

S	R	Q	Q_next	Q'_next
0	0	0	0	1
1	0	0	1	0
0	0	1	1	0




# 🔥 SR latch with NOR gates

A	B	A NOR B
1	1	0
1	0	0
0	1	0
0	0	1

- We have seen an SR (Set-Reset) latch using NAND.
  - An SR latch can also be built from NOR gates.

How does this work?

 


S	R	Q	Q_next	Q'_next
0	0	0	0	1
1	0	0	1	0
0	0	1	1	0
0	1	1		

# 🔥 SR latch with NOR gates

A	B	A NOR B
1	1	0
1	0	0
0	1	0
0	0	1

- We have seen an SR (Set-Reset) latch using NAND.
  - An SR latch can also be built from NOR gates.

How does this work?

 


S	R	Q	Q_next	Q'_next
0	0	0	0	1
1	0	0	1	0
0	0	1	1	0
0	1	1	0	1

# 🔥 SR latch with NOR gates

A	B	A NOR B
1	1	0
1	0	0
0	1	0
0	0	1

- We have seen an SR (Set-Reset) latch using NAND.
  - An SR latch can also be built from NOR gates.

How does this work?

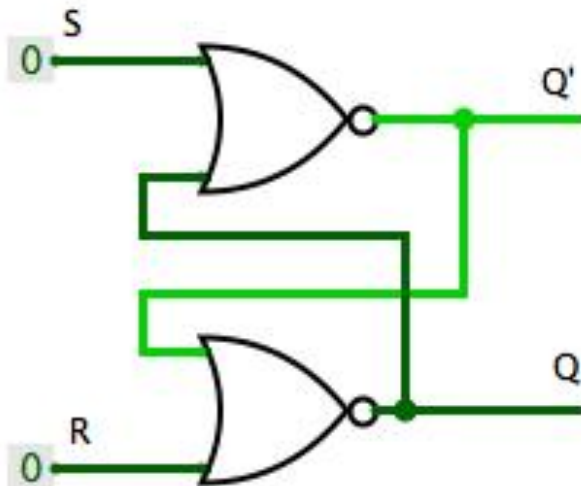


S	R	Q	Q_next	Q'_next
0	0	0	0	1
1	0	0	1	0
0	0	1	1	0
0	1	1	0	1
0	0	0		

# 🔥 SR latch with NOR gates

A	B	A NOR B
1	1	0
1	0	0
0	1	0
0	0	1

- We have seen an SR (Set-Reset) latch using NAND.
  - An SR latch can also be built from NOR gates.

How does this work?

 


S	R	Q	Q_next	Q'_next
0	0	0	0	1
1	0	0	1	0
0	0	1	1	0
0	1	1	0	1
0	0	0	0	1

# 🔥 SR latch with NOR gates

A	B	A NOR B
1	1	0
1	0	0
0	1	0
0	0	1

- We have seen an SR (Set-Reset) latch using NAND.
  - An SR latch can also be built from NOR gates.

How does this work?

 


S	R	Q	Q_next	Q'_next
0	0	0	0	1
1	0	0	1	0
0	0	1	1	0
0	1	1	0	1
0	0	0	0	1

# 🔥 SR latch with NOR gates

A	B	A NOR B
1	1	0
1	0	0
0	1	0
0	0	1

- We have seen an SR (Set-Reset) latch using NAND.
  - An SR latch can also be built from NOR gates.

How does this work?

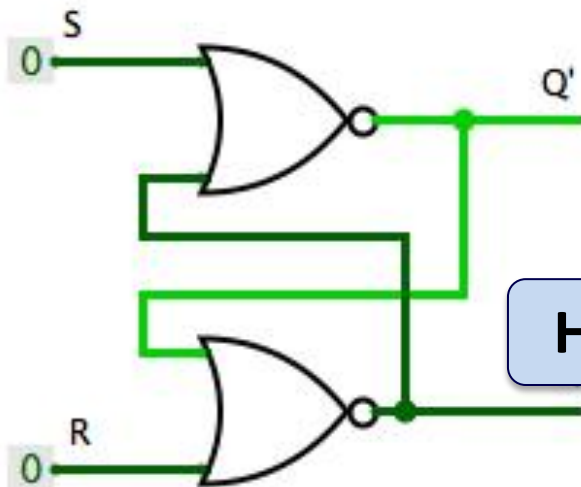


S	R	Q	Q_next	Q'_next
0	0	0	0	1
1	0	0	1	0
0	0	1	1	0
0	1	1	0	1
0	0	0	0	1

# 🔥 SR latch with NOR gates

A	B	A NOR B
1	1	0
1	0	0
0	1	0
0	0	1

- We have seen an SR (Set-Reset) latch using NAND.
  - An SR latch can also be built from NOR gates.

How does this work?

 

**RESET**

S	R	Q	Q_next	Q'_next
0	0	0	0	1
1	0	0	1	0
0	0	1	1	0
0	1	1	0	1
0	0	0	0	1




# 🔥 SR latch with NOR gates

A	B	A NOR B
1	1	0
1	0	0
0	1	0
0	0	1

- We have seen an SR (Set-Reset) latch using NAND.
  - An SR latch can also be built from NOR gates.

How does this work?

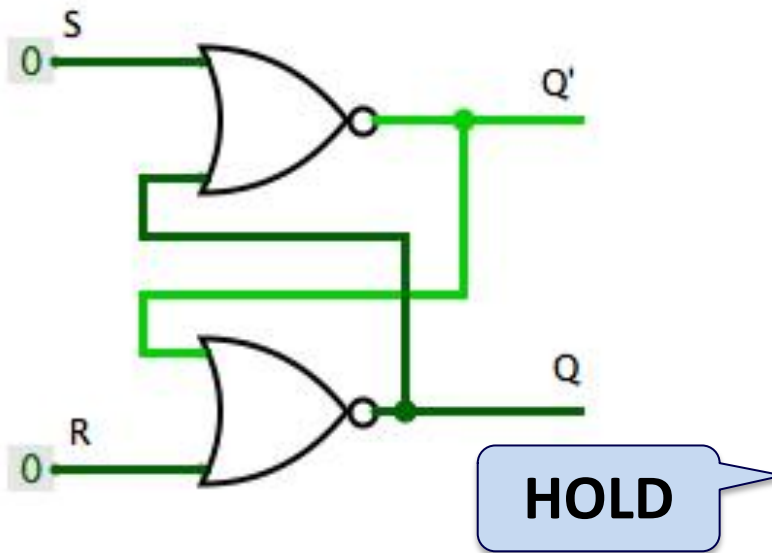


S	R	Q	Q_next	Q'_next
0	0	0	0	1
1	0	0	1	0
0	0	1	1	0
0	1	1	0	1
0	0	0	0	1



# 🔥 SR latch with NOR gates

A	B	A NOR B
1	1	0
1	0	0
0	1	0
0	0	1

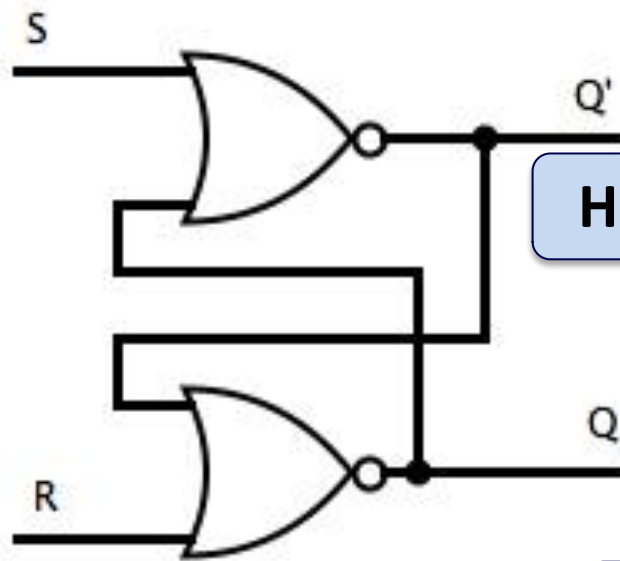- We have seen an SR (Set-Reset) latch using NAND.
  - An SR latch can also be built from NOR gates.



How does this work?

S	R	Q	Q'
0	0	Q_prev	Q'_prev
0	1	0	1
1	0	1	0
1	1		

**HOLD** (points to the first row where S=0, R=0)


**SET** (points to the third row where S=1, R=0)

**RESET** (points to the second row where S=0, R=1)

# 🔥 SR latch with NOR gates

A	B	A NOR B
1	1	0
1	0	0
0	1	0
0	0	1

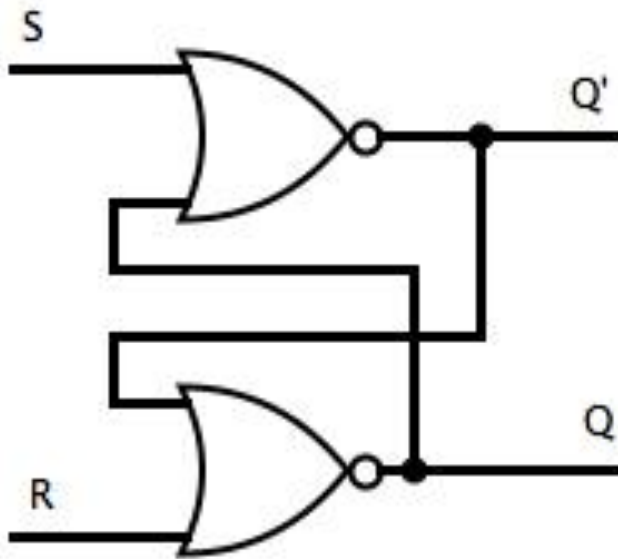- We have seen an SR (Set-Reset) latch using NAND.
  - An SR latch can also be built from NOR gates.



How does this work?

S	R	Q	Q'
0	0	Q_prev	Q'_prev
0	1	0	1
1	0	1	0
<b>1</b>	<b>1</b>	<b>not allowed</b>	


# Different latch types

- SR (Set-Reset) latch
  - using NAND gates
  - using NOR gates
- Other latches:
  - **D latch**
  - JK latch

# D-latch

- Instead of separate set/reset inputs, one input, **D**, specifies the **data** value, and a second input, **E**, **enables** propagation.
- If E is low, the previous output values are retained.


D	E	Q	Q'
0	0	Q_prev	Q'_prev
0	1	0	1
1	0	Q_prev	Q'_prev
1	1	1	0

 


# D-latch

- Instead of separate set/reset inputs, one input, **D**, specifies the **data** value, and a second input, **E**, **enables** propagation.
- If E is low, the previous output values are retained.
- No forbidden inputs.
  - Why?

D	E	Q	Q'
0	0	Q_prev	Q'_prev
0	1	0	1
1	0	Q_prev	Q'_prev
1	1	1	0

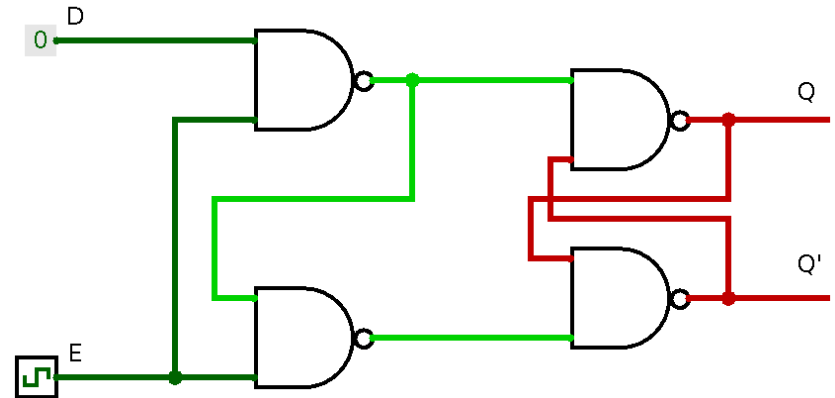

# 🔥 D-latch internal signals

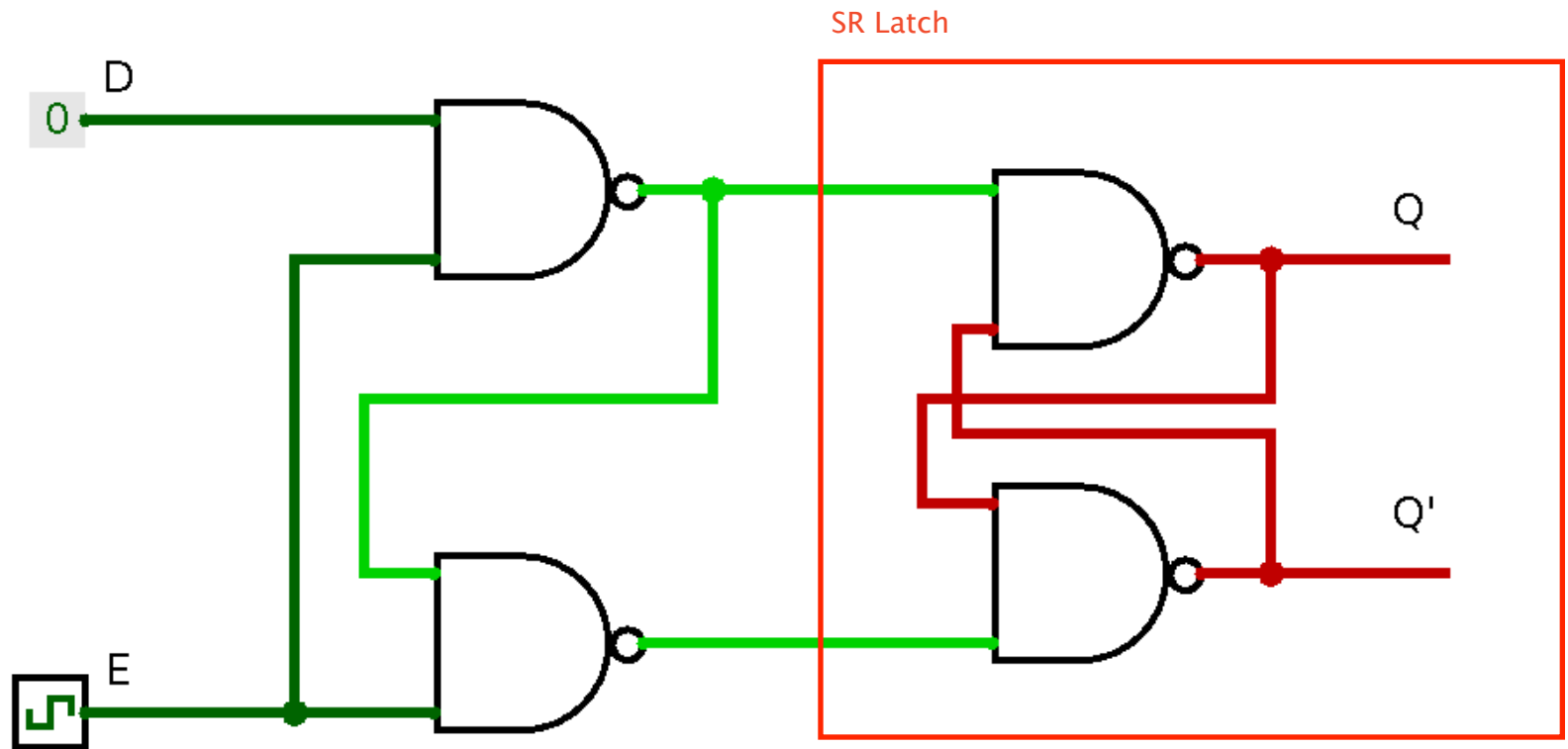

# 🔥 D-latch truth table - I



$D$	$E$	$\bar{S}$	$\bar{R}$	$Q$	$\bar{Q}$
0	0	1	1	HOLD	
0	1	1	0	0	1
1	0	1	1	HOLD	
1	1	0	1	1	0



# 🔥 D-latch truth table - II



$D$	$E$	$\bar{S}$	$\bar{R}$	$Q$	$\bar{Q}$
0	0	1	1		
0	1	1	0		
1	0	1	1		
1	1	0	1		





# 🔥 D-latch truth table - II

S'	R'	Q	Q'
1	1	hold	
1	0	0	1
0	1	1	0
0	0	Not allowed	

D	E	$\bar{S}$	$\bar{R}$	Q	$\bar{Q}$
0	0	1	1		
0	1	1	0		
1	0	1	1		
1	1	0	1		

# 🔥 D-latch truth table - III

S'	R'	Q	Q'
1	1	hold	
1	0	0	1
0	1	1	0
0	0	Not allowed	





D	E	$\bar{S}$	$\bar{R}$	Q	$\bar{Q}$
0	0	1	1	hold	
0	1	1	0	0	1
1	0	1	1	hold	
1	1	0	1	1	0

# 🔥 D-latch truth table - III


S'	R'	Q	Q'
1	1	hold	
1	0	0	1
0	1	1	0
0	0	Not allowed	

D	E	$\bar{S}$	$\bar{R}$	Q	$\bar{Q}$
0	0	1	1	hold	
0	1	1	0	0	1
1	0	1	1	hold	
1	1	0	1	1	0


# 🔥 D-latch simulation

    


# Waveform

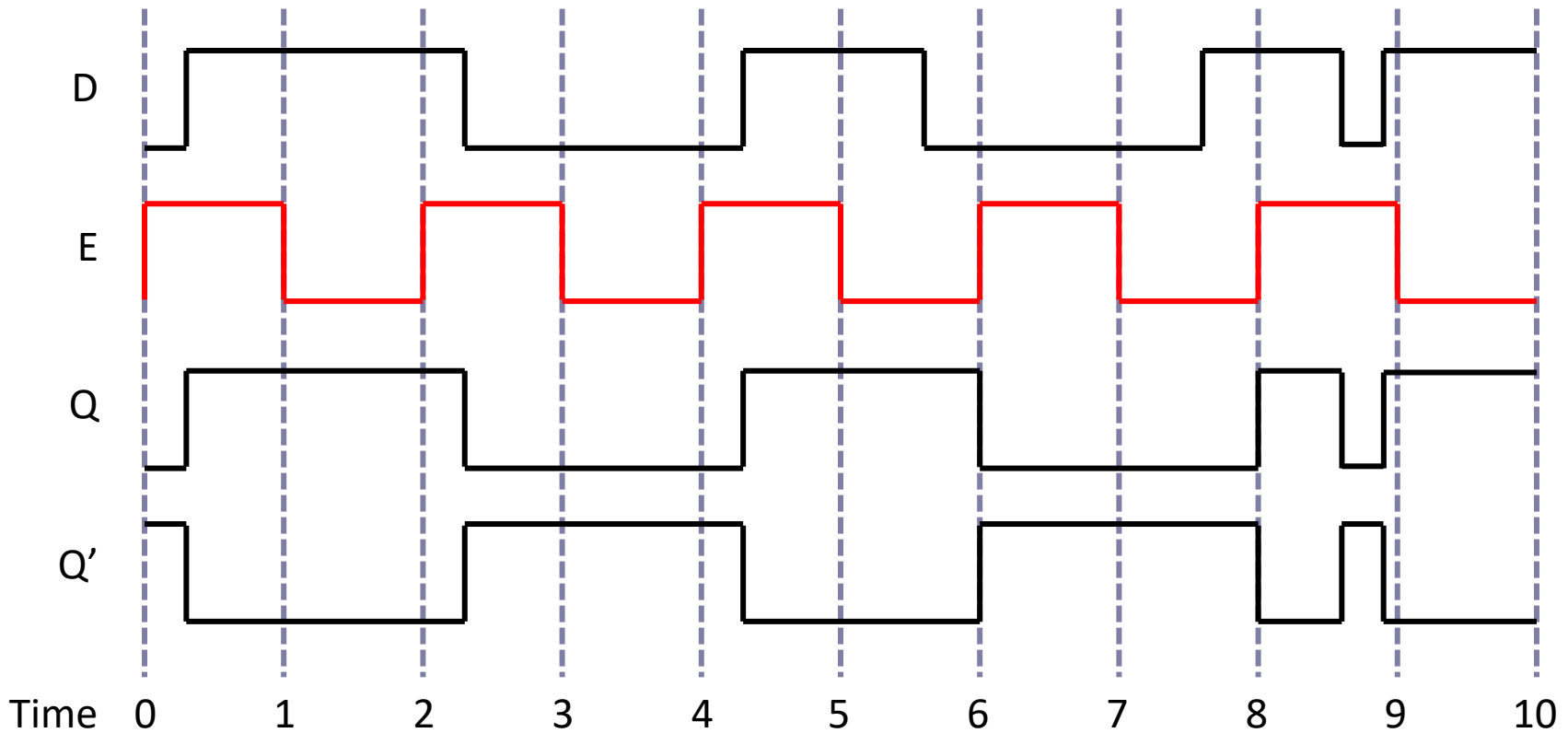

# Waveform

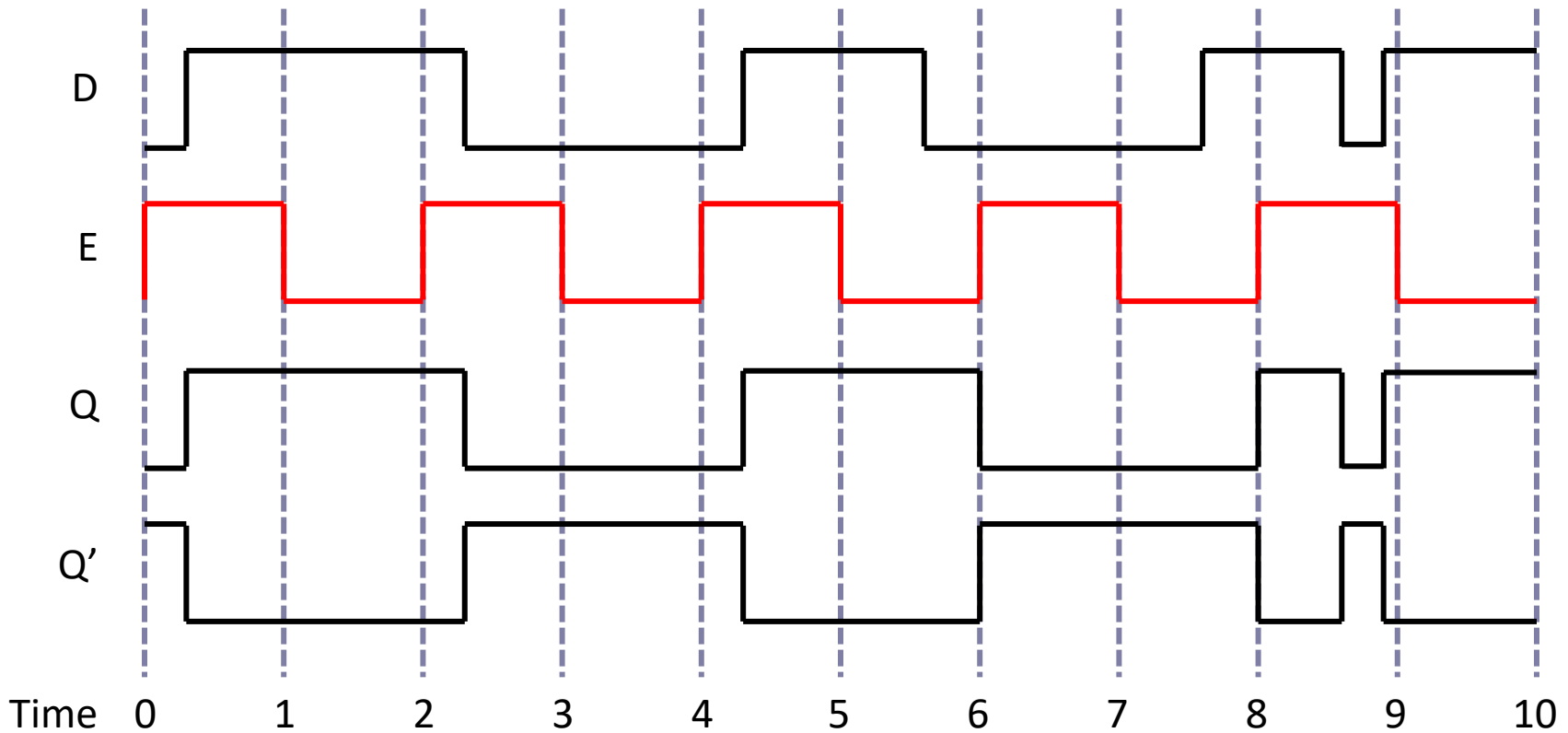


# Waveform

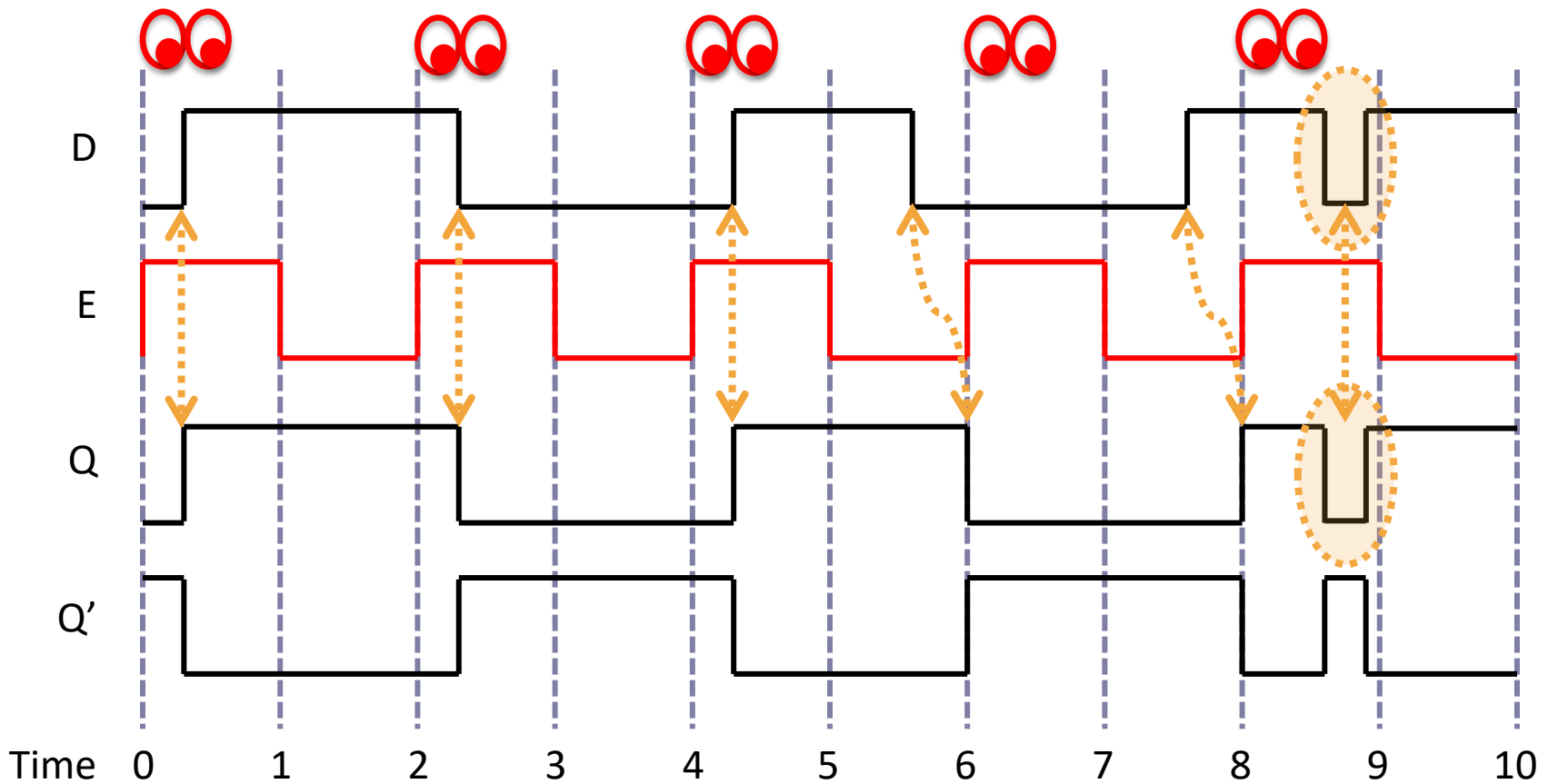
 
# 🔥 Level vs. edge triggering


- **Latches** are *level* sensitive.
- We can also build *edge* sensitive devices - **Flip-flops**





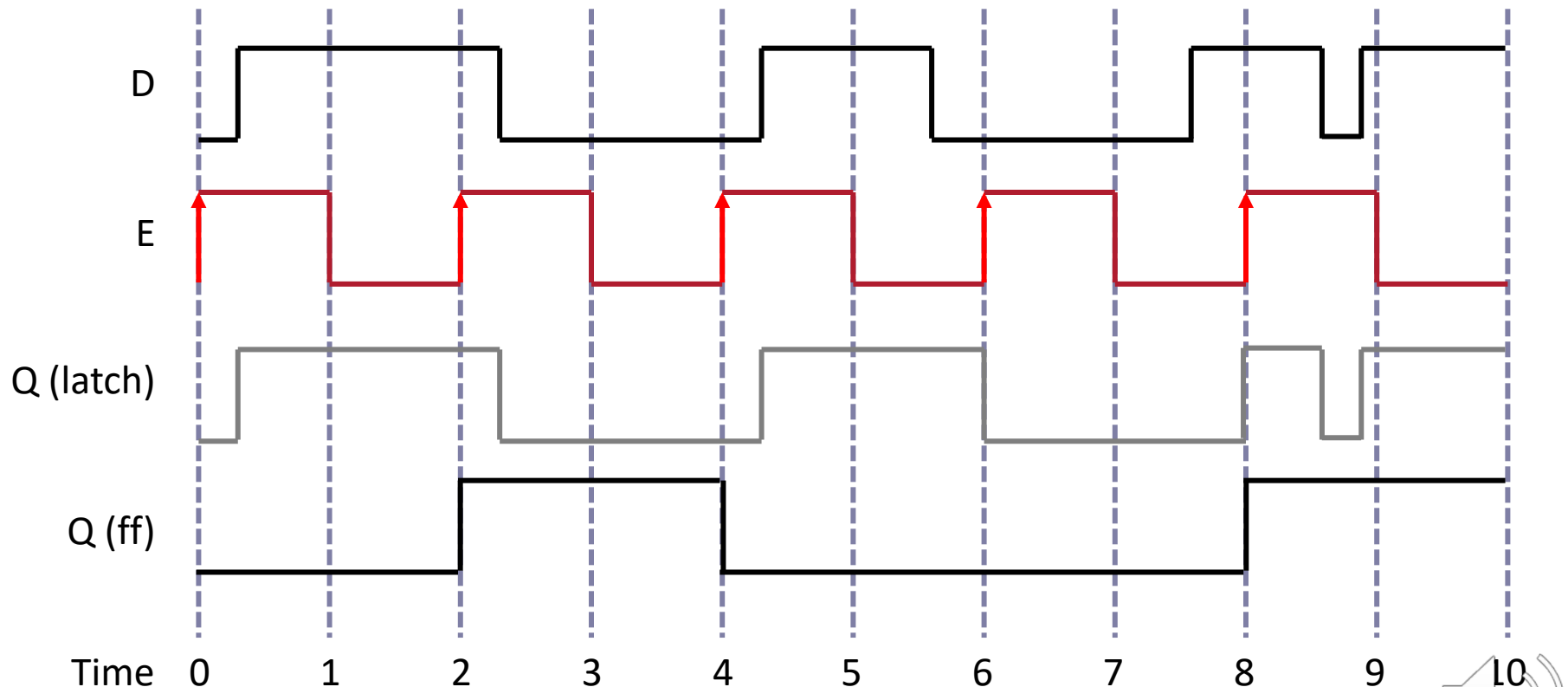
# 🔥 Level vs. edge triggering

- Latches are *level* sensitive.
- We can also build *edge* sensitive devices - Flip-flops



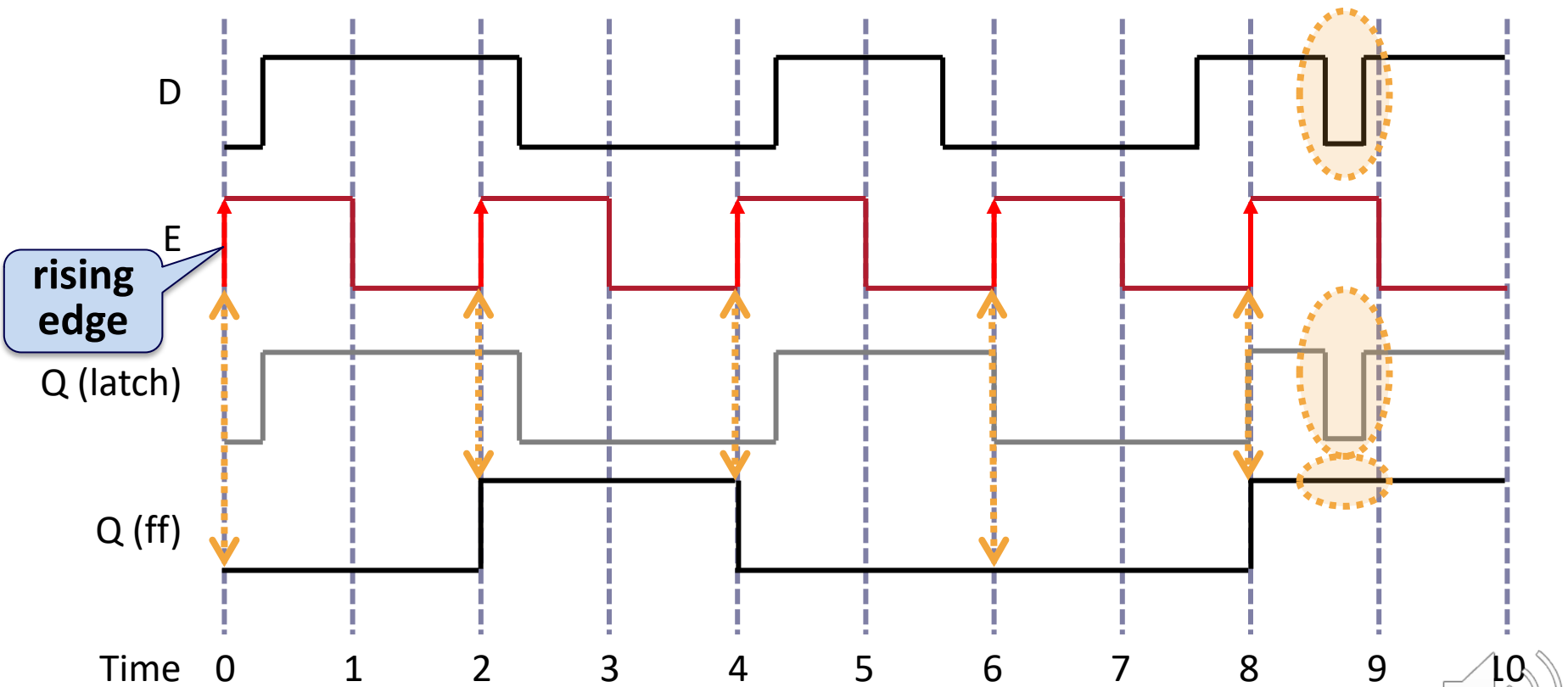
# 🔥 Level vs. edge triggering

- Latches are *level* sensitive.
- We can also build *edge* sensitive devices - Flip-flops




# 🔥 Building a D-type flip-flop

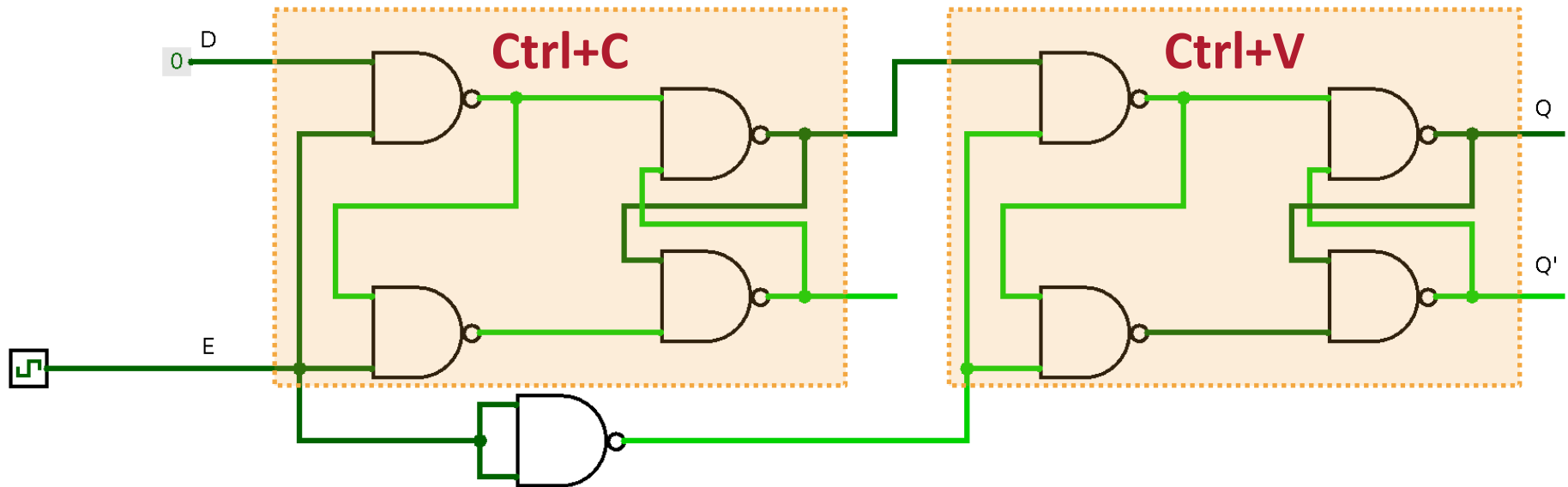

- Two D-type latches.
- Inverted enable signal to the second latch.
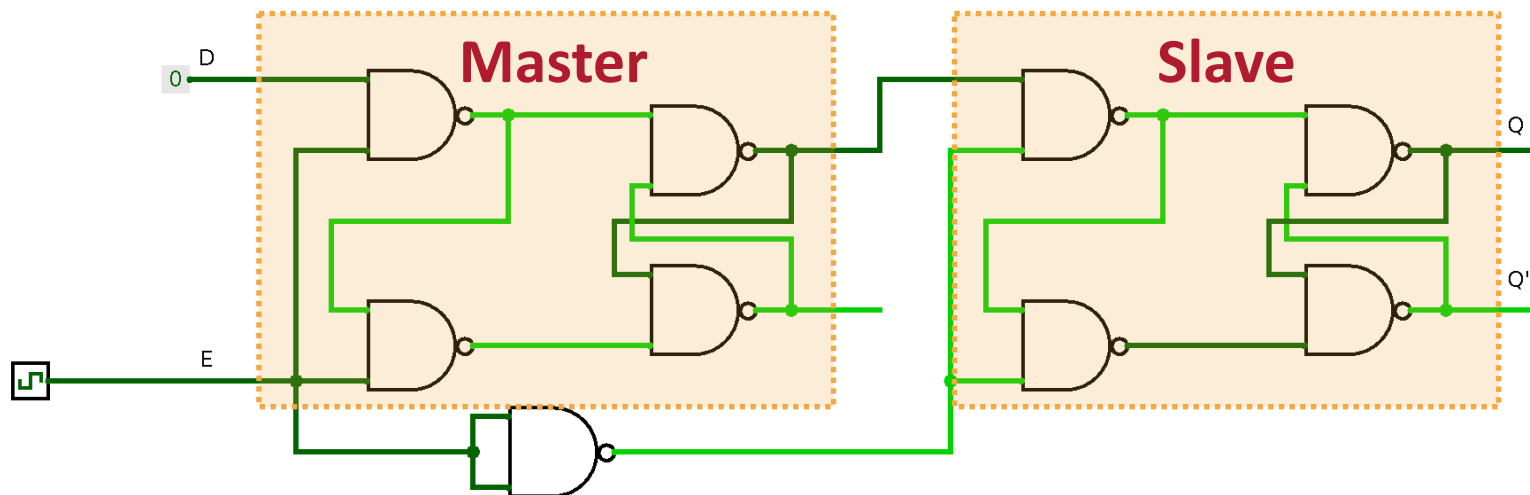
# 🔥 Building a D-type flip-flop


- The example shown is a master-slave D-type flip-flop.
- The master latch is enabled on E high.
  - The slave is disabled, its output is **held**.
- The slave latch is enabled on E low.
  - The master is disabled, its output is held.



# 🔥 D-type flip-flop transition



## What have we built?

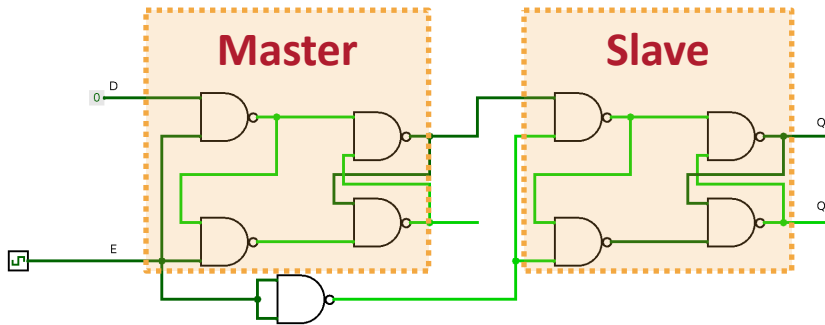


D	E >	Q
0	Rising	Q_prev
0	Falling	0
1	Rising	Q_prev
1	Falling	1



# 🔥 D-type flip-flop transition


## What have we built?

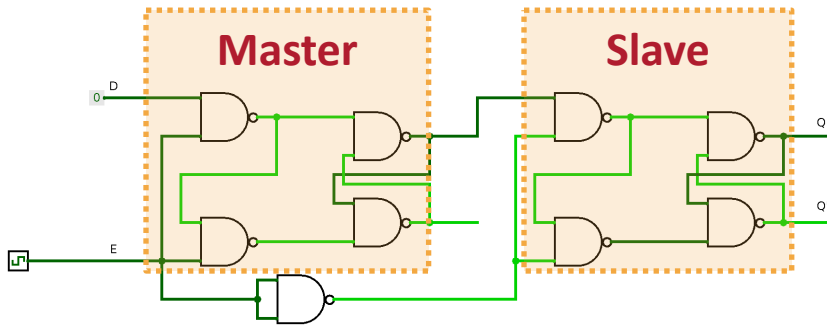

D	E >	Q
0	Rising	Q_prev
0	Falling	0
1	Rising	Q_prev
1	Falling	1


- We have built a **falling-edge** or **negative-edge triggered** flip-flop.
  - Note, the timing diagram earlier demonstrated *positive edge* behaviour.
- There is **more than one way** to make a D-type FF.
  - Explore different designs in the next NAND lab.
- How would we make it **positive-edge**?
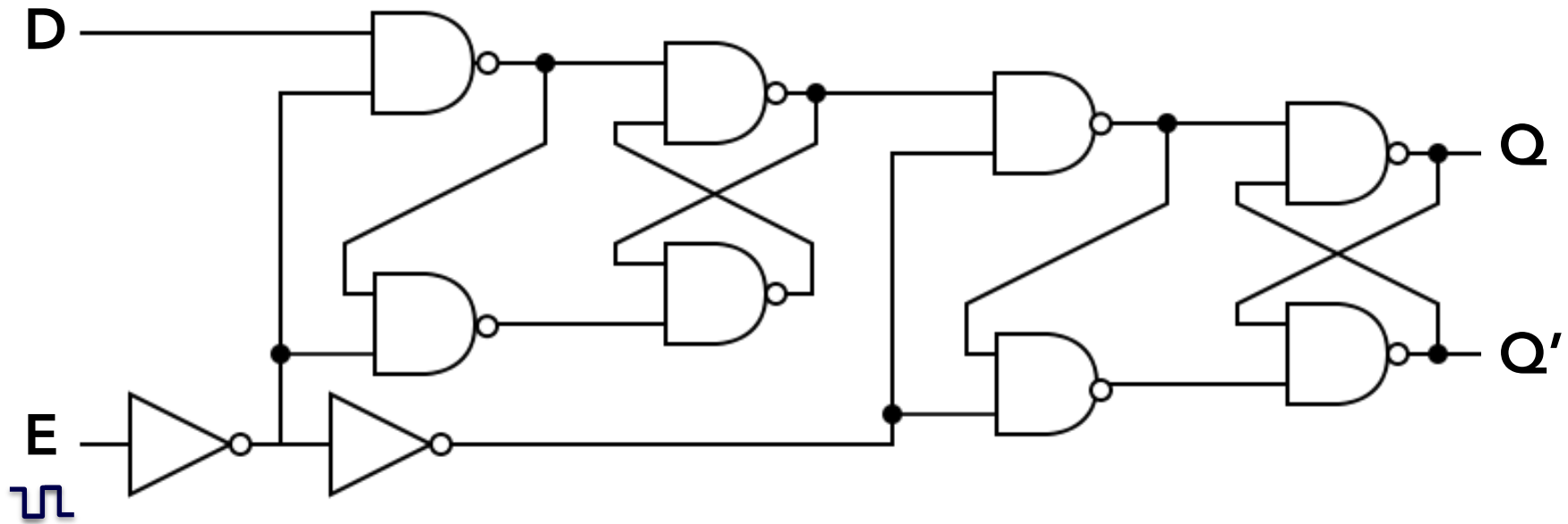
# 🔥 How can we make it **positive-edge**?



... by adding an inverter that negates the enable signal, E.

 
# 🔥 How can we make it **positive-edge**?



... by adding an inverter that negates the enable signal, E.




# Timing

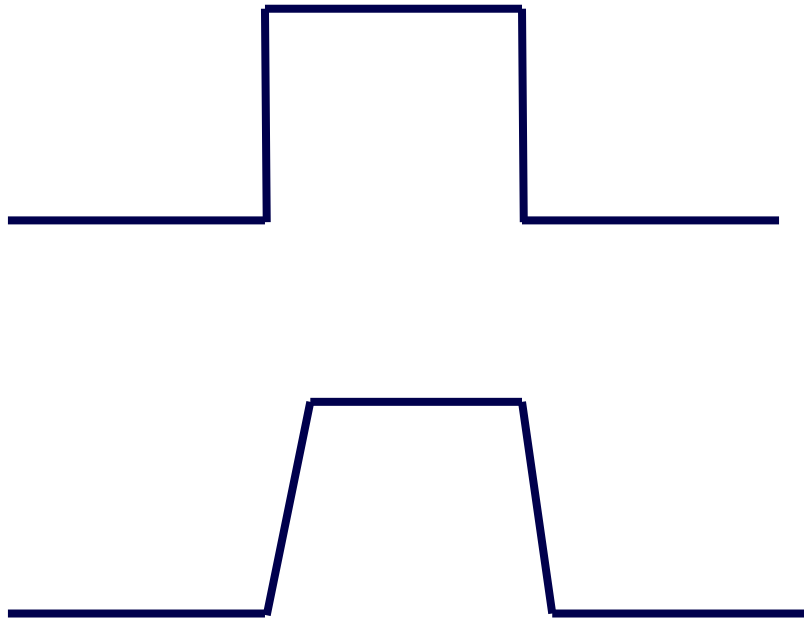

- We imagine signal transitions as instant.
- But they're not!
  - Wires and transistors have capacitances.
  - They have a charge/discharge time.
  - Remember the Ring Oscillator!




# 🔥 Timing: rise times

 


- We imagine signal transitions as instant.
- But they're not!
  - Wires and transistors have capacitances.
  - They have a charge/discharge time.
  - Remember the Ring Oscillator!
- This results in rise & fall times.

# 🔥 Timing: rise times and fall times

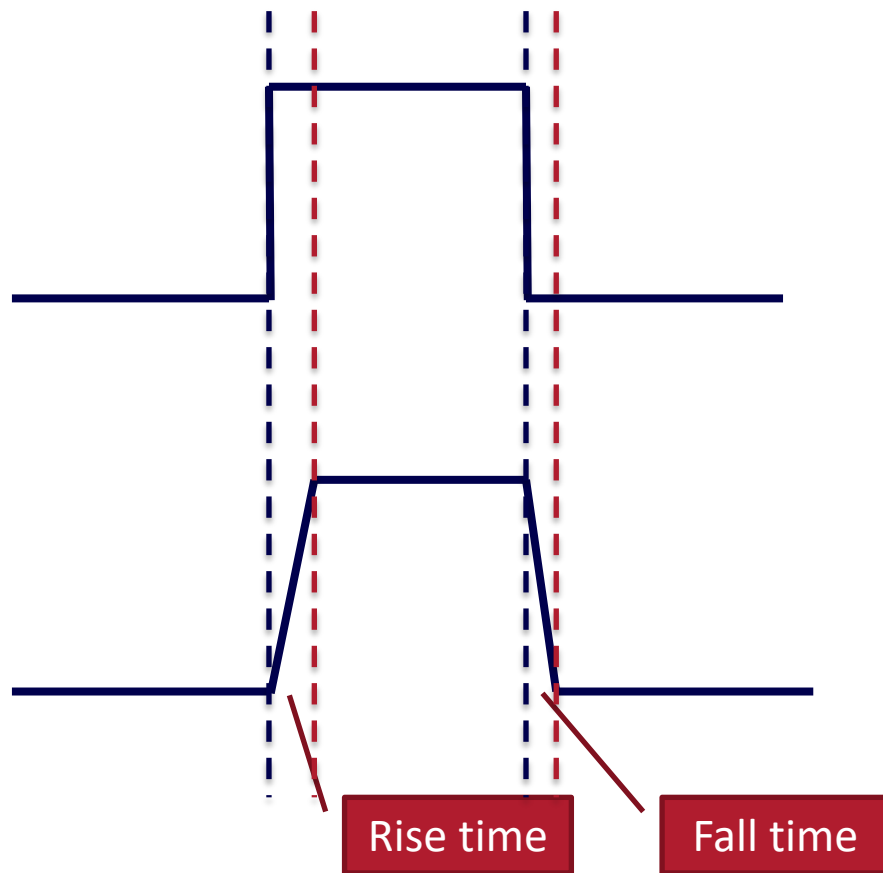

- We imagine signal transitions as instant.
- But they're not!
  - Wires and transistors have capacitances.
  - They have a charge/discharge time.
  - Remember the Ring Oscillator!
- This results in rise & fall times.

# 🔥 Timing: rise times and fall times

 

- When a signal changes there is a period of time where **we don't know its value**.
- So, if events (i.e. clock edges) happen at the wrong time, then **unexpected behaviour can occur**.

# 🔥 Timing constraints



*the  
event*

Clock

$t_{\text{setup}}$

$t_{\text{hold}}$

D

Q


$t_{\text{co}}$

We specify **timing constraints** to try to avoid these problems.

- Setup time ( $t_{\text{setup}}$ )
  - How long the signal should be settled **before** the **event**, e.g. rising clock edge.
- Hold time ( $t_{\text{hold}}$ )
  - How long the signal should remain settled **after** the **event**.
- Clock-to-output ( $t_{\text{co}}$ )
  - The time between the **event** and the **output changing**.




# 🔥 Timing constraints

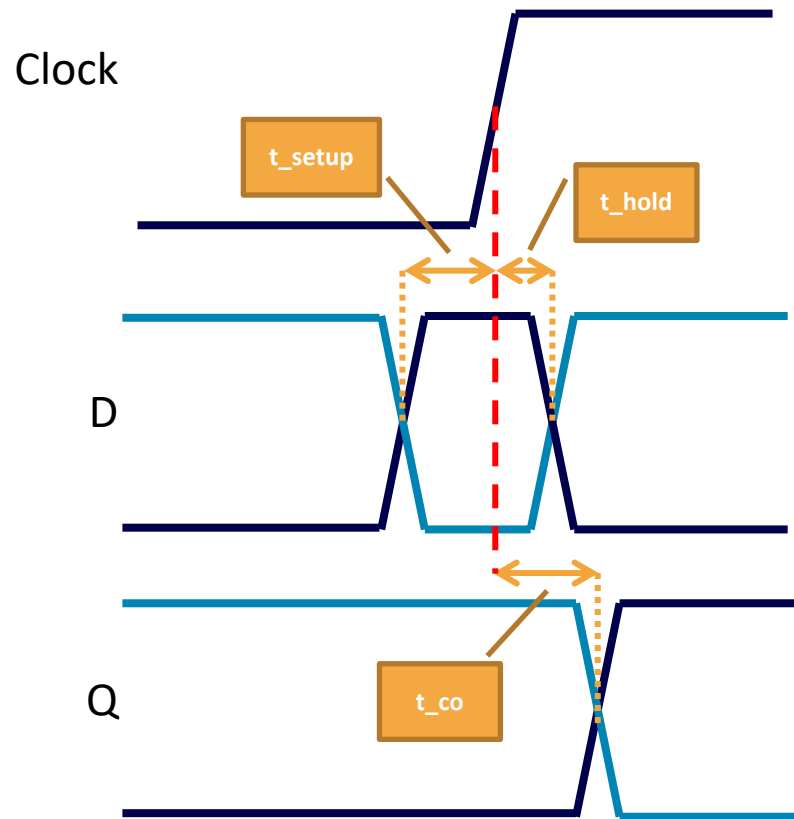

- We specify **timing constraints** to try to avoid these problems.
- Setup time ( $t_{\text{setup}}$ )
  - How long the signal should be settled **before** the **event**, e.g. rising clock edge.
- Hold time ( $t_{\text{hold}}$ )
  - How long the signal should remain settled **after** the **event**.
- Clock-to-output ( $t_{\text{co}}$ )
  - The time between the **event** and the **output changing**.
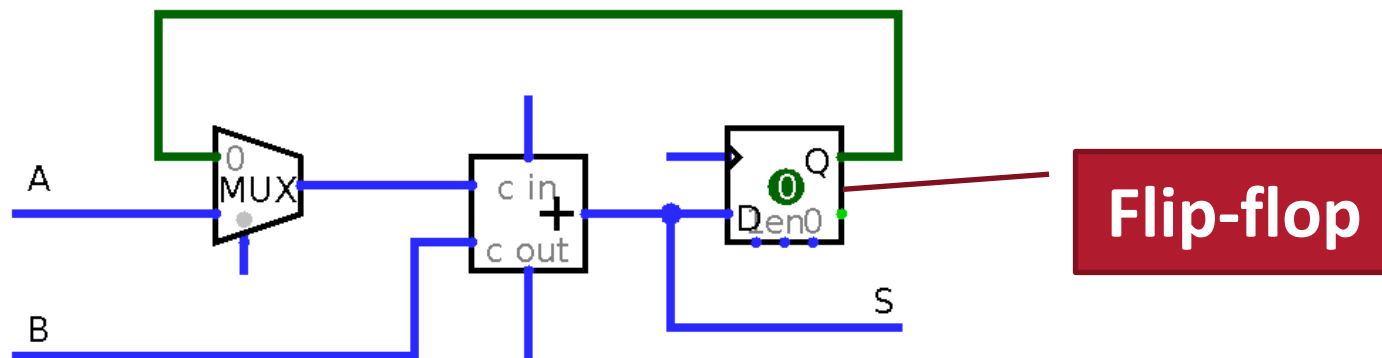
# 🔥 Combinatorial vs. sequential logic

- To enforce a sequence reliably, we can:
  - Store result values
  - Control when values are stored
- This allows us to build a sequential system, combining **storage** and **combinatorial logic**.



# What have we got now?

- We have enough devices to perform **sequences of operations**.
  - Results can be **stored and reused** in the next operation.
  - We have to set or reset our inputs **by hand** at each stage in the sequence.
  - We have a **clock** that we have to operate **by hand**.
- We have flip-flops – single units of **memory**.
  - Soon we will have more complex memories.
  - And ways of controlling the system **without** manual (by hand) intervention.





# In this lecture

## Foundations

- Data representation, logic, Boolean algebra.

## Building blocks

- Transistors, transistor based logic, simple devices, **storage**.

## Modules

- Memory, simple controllers, FSMs, processors and execution.

## Programming

- Machine code, assembly, high-level languages, compilers.

## Wrap-up

- Operating systems, energy aware computing.



# In the next lecture

## Foundations

- Data representation, logic, Boolean algebra.

## Building blocks

- Transistors, transistor based logic, simple devices, storage.

## Modules

- **Memory**, simple controllers, FSMs, processors and execution.

## Programming

- Machine code, assembly, high-level languages, compilers.

## Wrap-up

- Operating systems, energy aware computing.

