

# COMSM1302

## Overview of Computer Architecture

### Lecture 9

### ModuleSim



# In the previous lecture

1. Computer systems layers.
2. 4-bit CPU from 4-bit counter.
3. ModuleSim simulation software

# In this lecture


## 1. Modulesim

1. Bus in Modulesim
2. Different components in ModuleSim
3. Solve some design problems

## 2. At the end of this lecture:

1. To use ModuleSim to implement and test your designs.


# Simulation

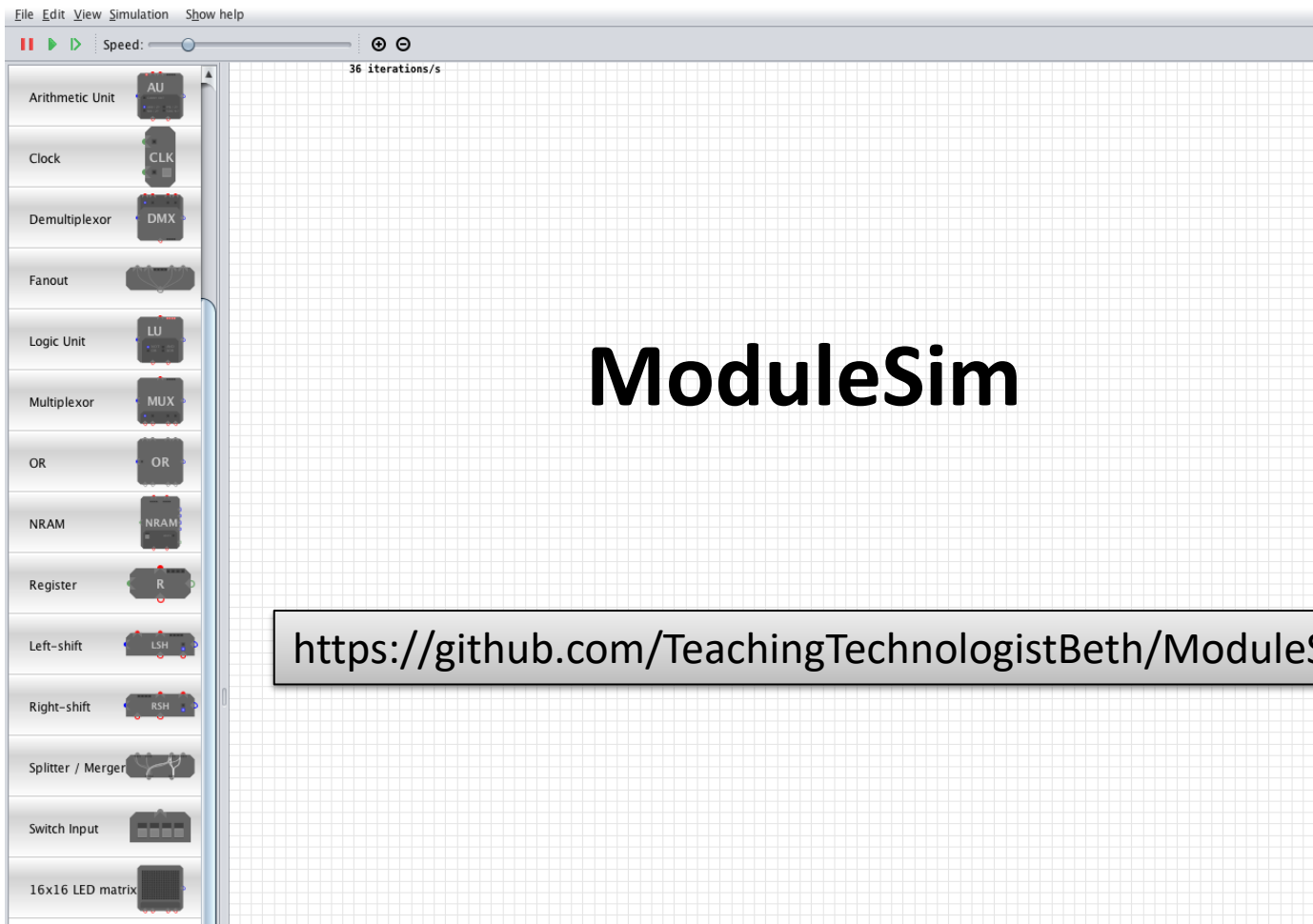


## ModuleSim


<https://github.com/TeachingTechnologistBeth/ModuleSim/releases>

# Bus

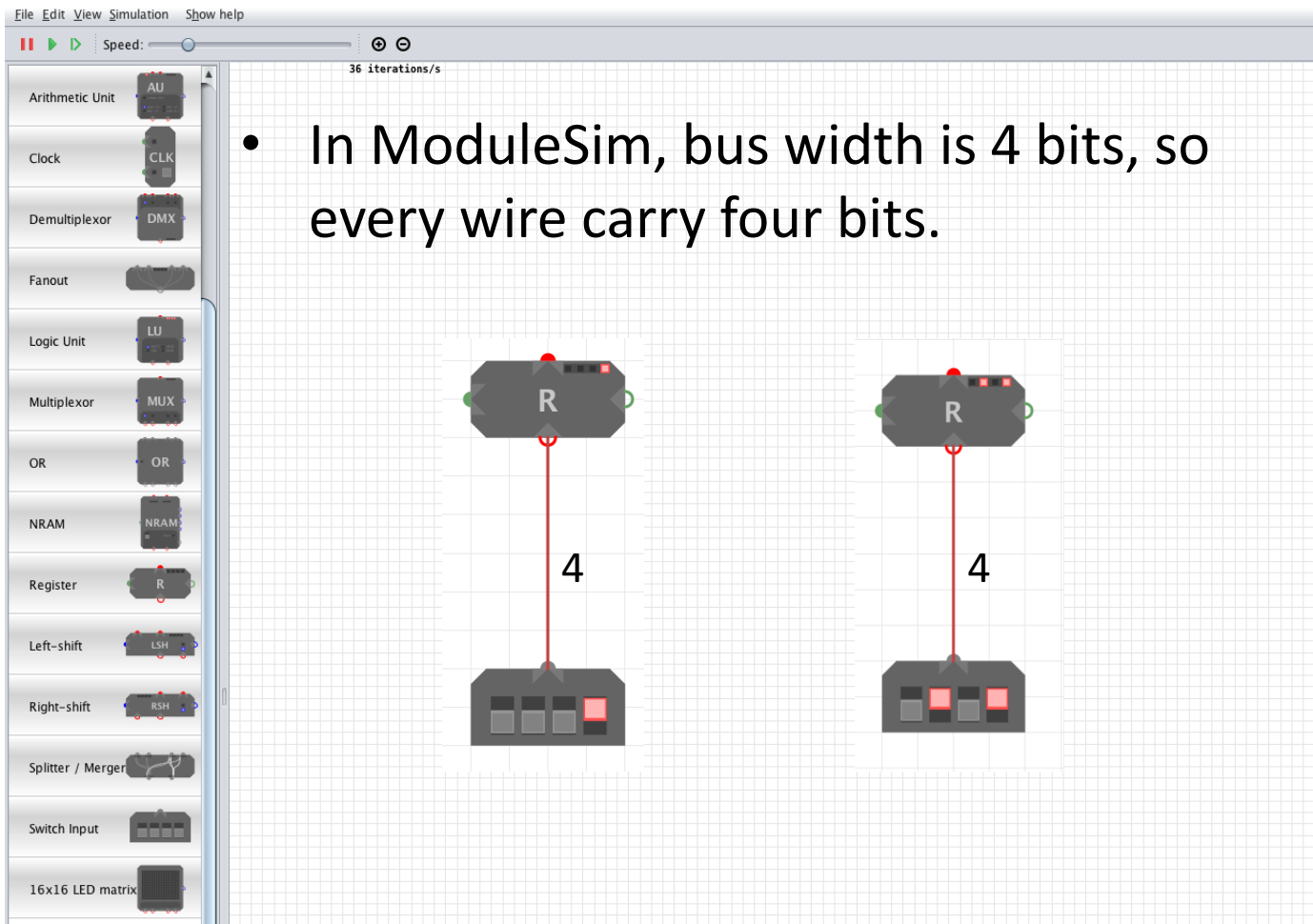


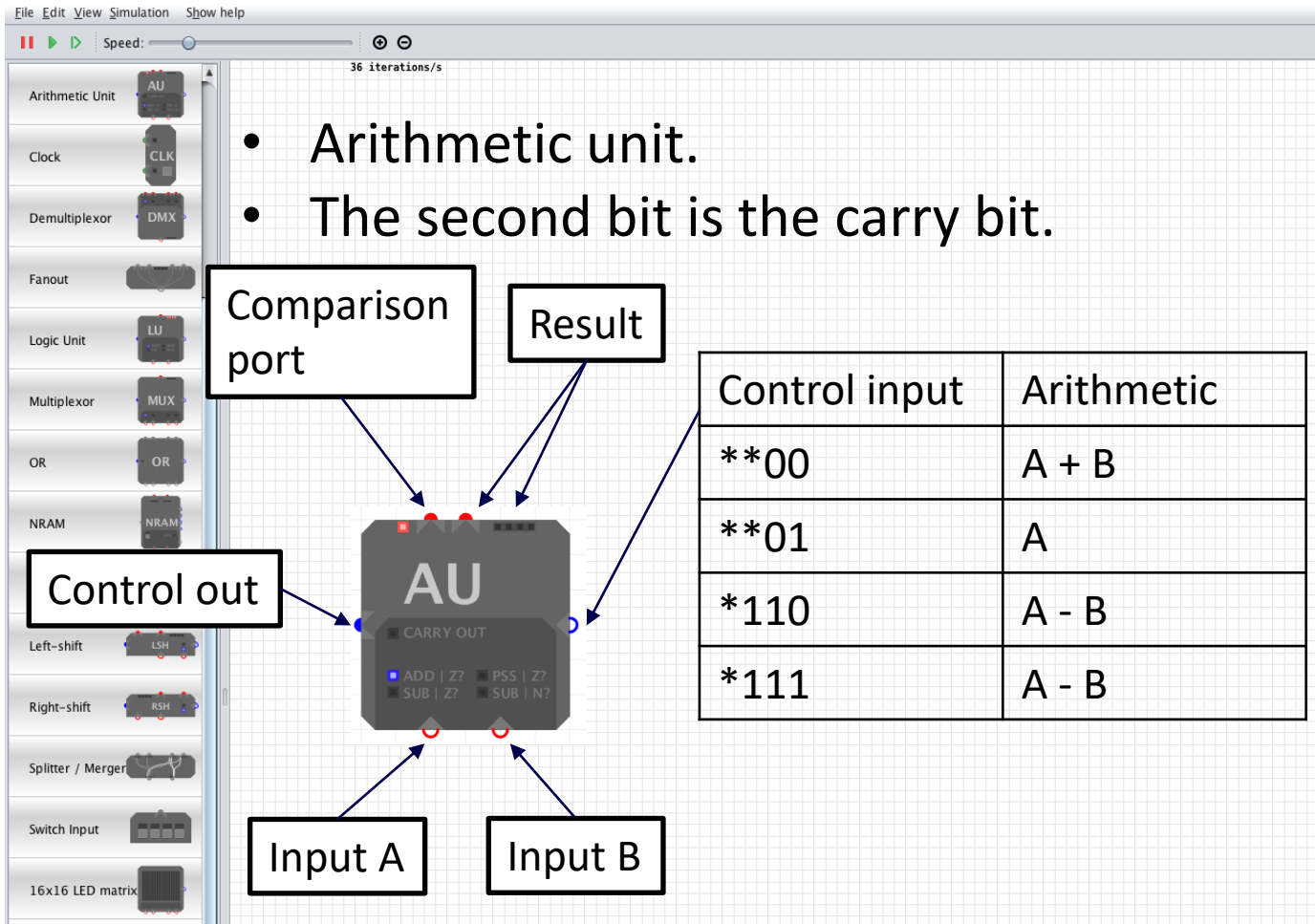

# Register

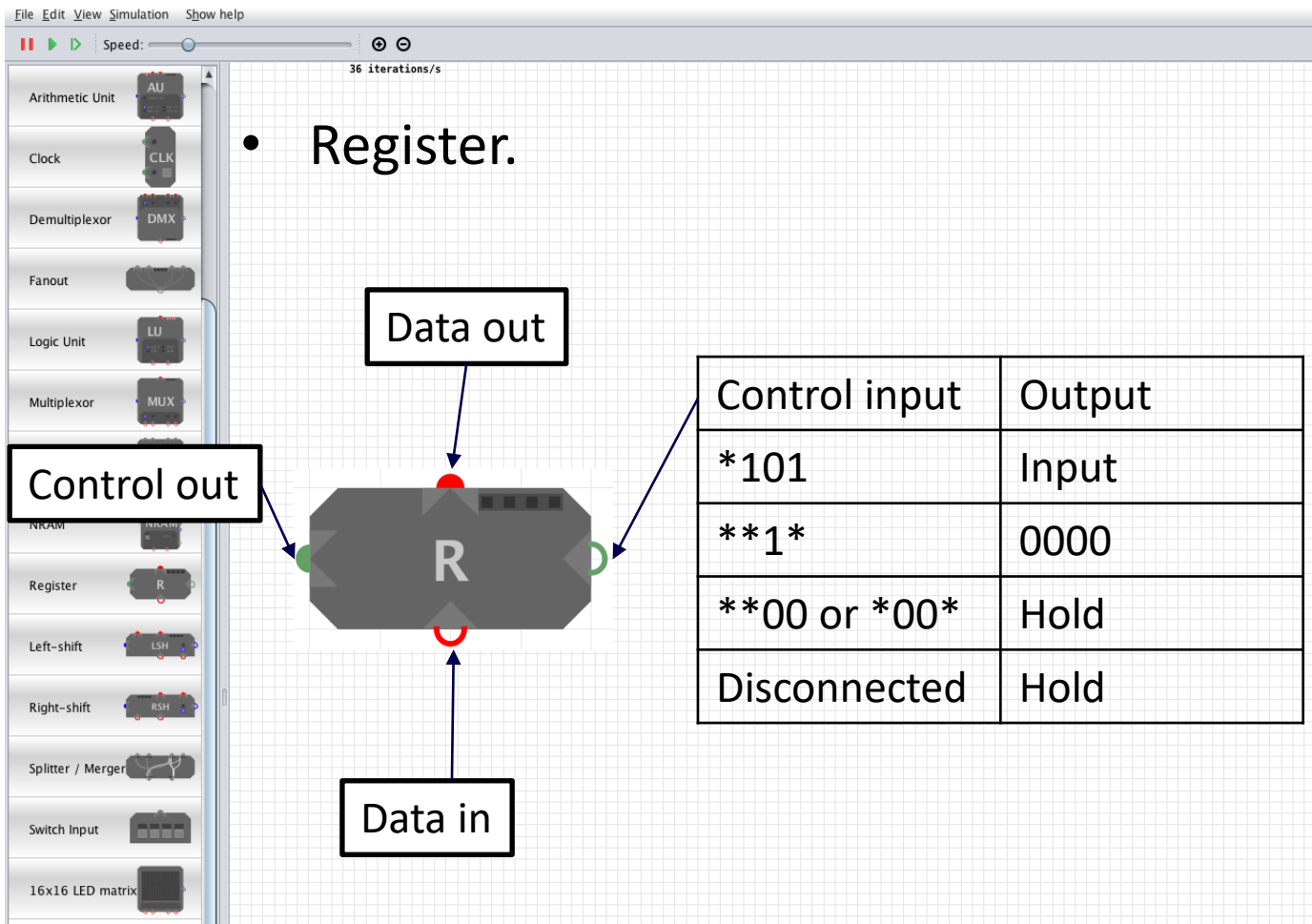

# Clock

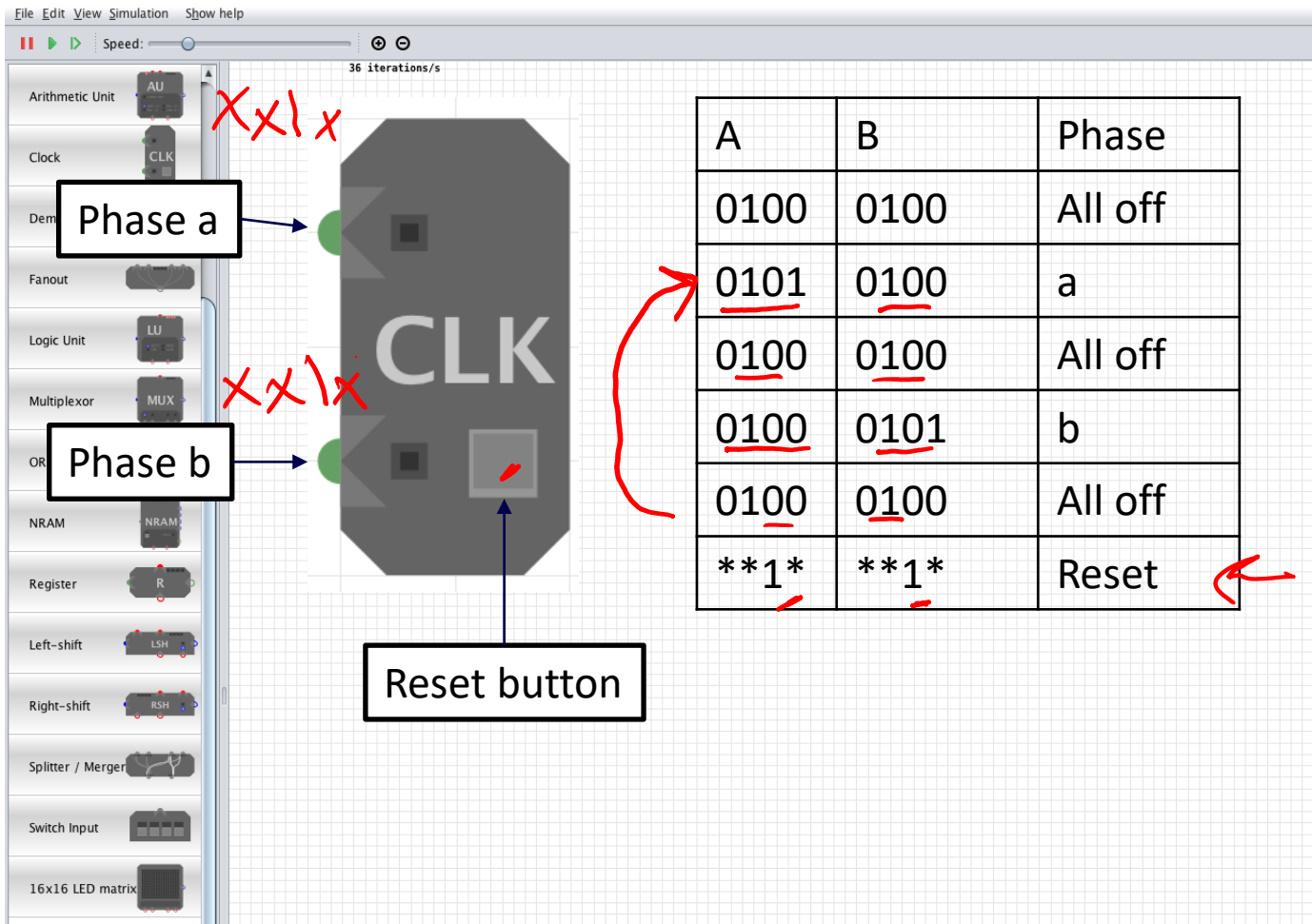




# Clock use

File Edit View Simulation Show help  
Speed: 36 iterations/s


A	B	Phase
0100	0100	All off
0101	0100	a
0100	0100	All off
0100	0101	b
0100	0100	All off
**1*	**1*	Reset

Registers control input	Output
*101	Input
**1*	0000
**00 or *00*	Hold

 

# Split/Merge

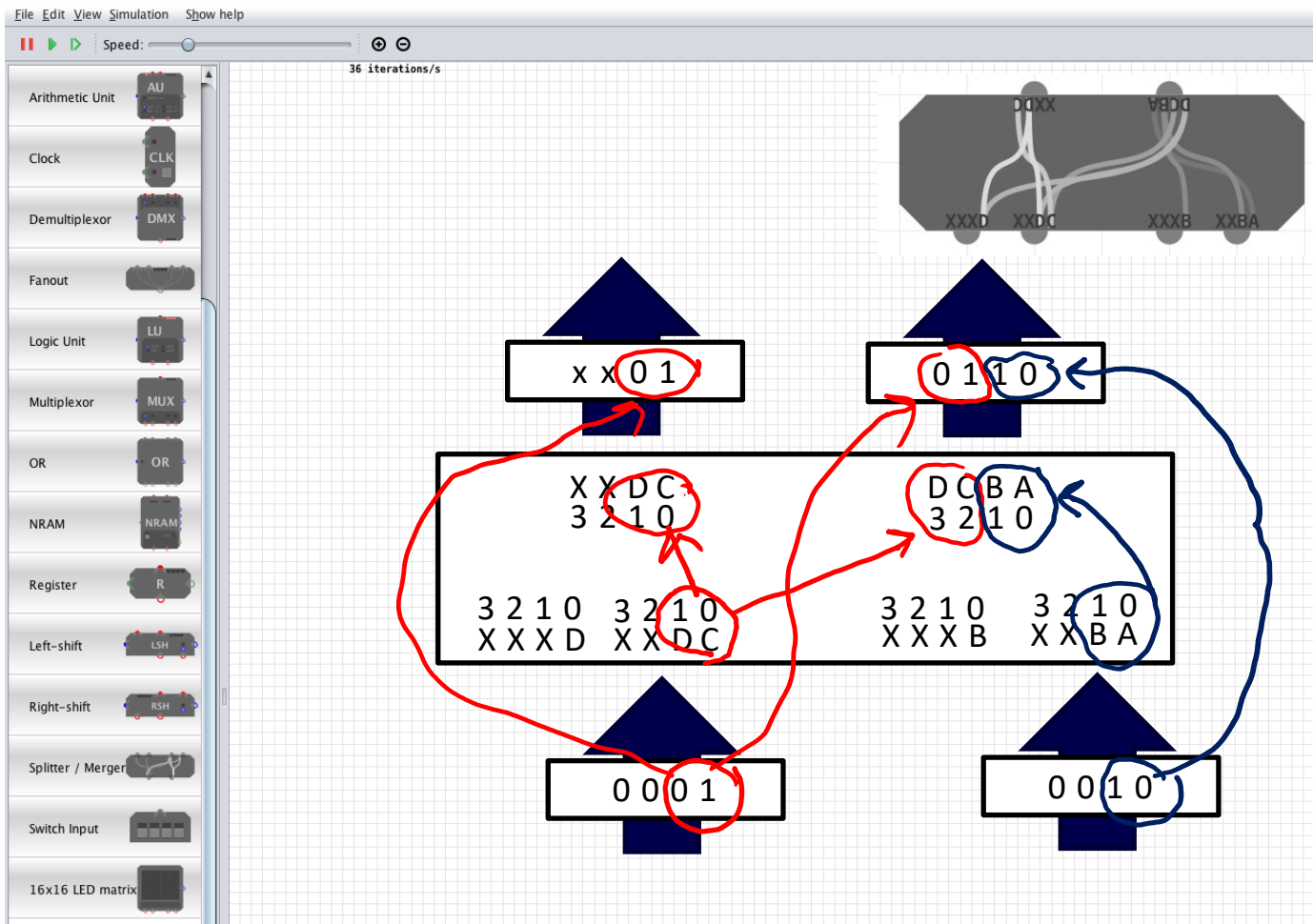

# Split/Merge – use 2-1



File Edit View Simulation Show help

Speed: 36 iterations/s

Arithmetic Unit AU

Clock CLK

Demultiplexor DMX

Fanout

Logic Unit LU

Multiplexor MUX

OR

NRAM

Register R

Left-shift LSH


Right-shift RSH

Splitter / Merger



Switch Input

16x16 LED matrix

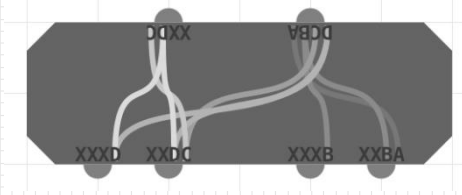2. Use this split/merge module to merge the first two bits from one 4-bit signal  $1_3 1_2 1_1 1_0$  with the first two bits from another 4-bit signal  $2_3 2_2 2_1 2_0$  into one signal  $2_1 2_0 1_1 1_0$ .



# Split/Merge – use 2-2

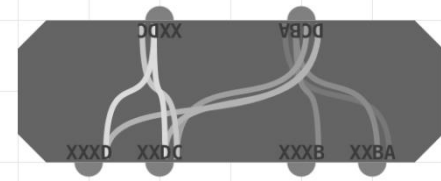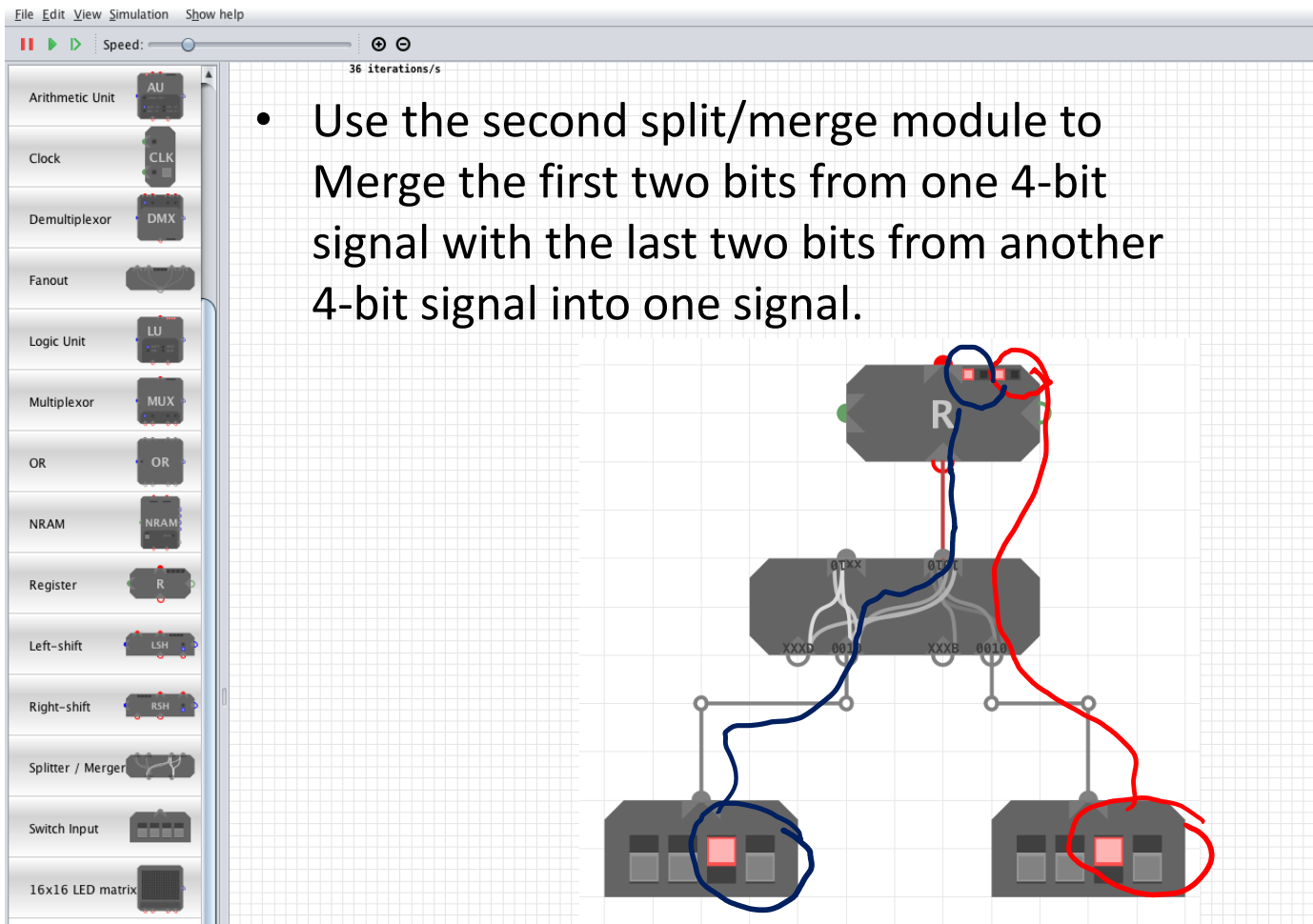

# Split/Merge – use 1-1

File Edit View Simulation Show help

Speed: 

36 iterations/s

Arithmetic Unit AU

Clock CLK

Demultiplexor DMX

Fanout

Logic Unit LU

Multiplexor MUX

OR

NRAM

Register R

Left-shift LSH


Right-shift RSH

Splitter / Merger



Switch Input

16x16 LED matrix

 
1. Use the first split/merge to split a 4-bit signal  $1_3 1_2 1_1 1_0$  to 2-bit signals. Such that the first two bits (LSB's) of the signal are the first two bits of one signal  $xx 1_1 1_0$  and the two high bits of the original signal are first two bits of another signal  $xx 1_3 1_2$ .




# Split/Merge – use 1-2

 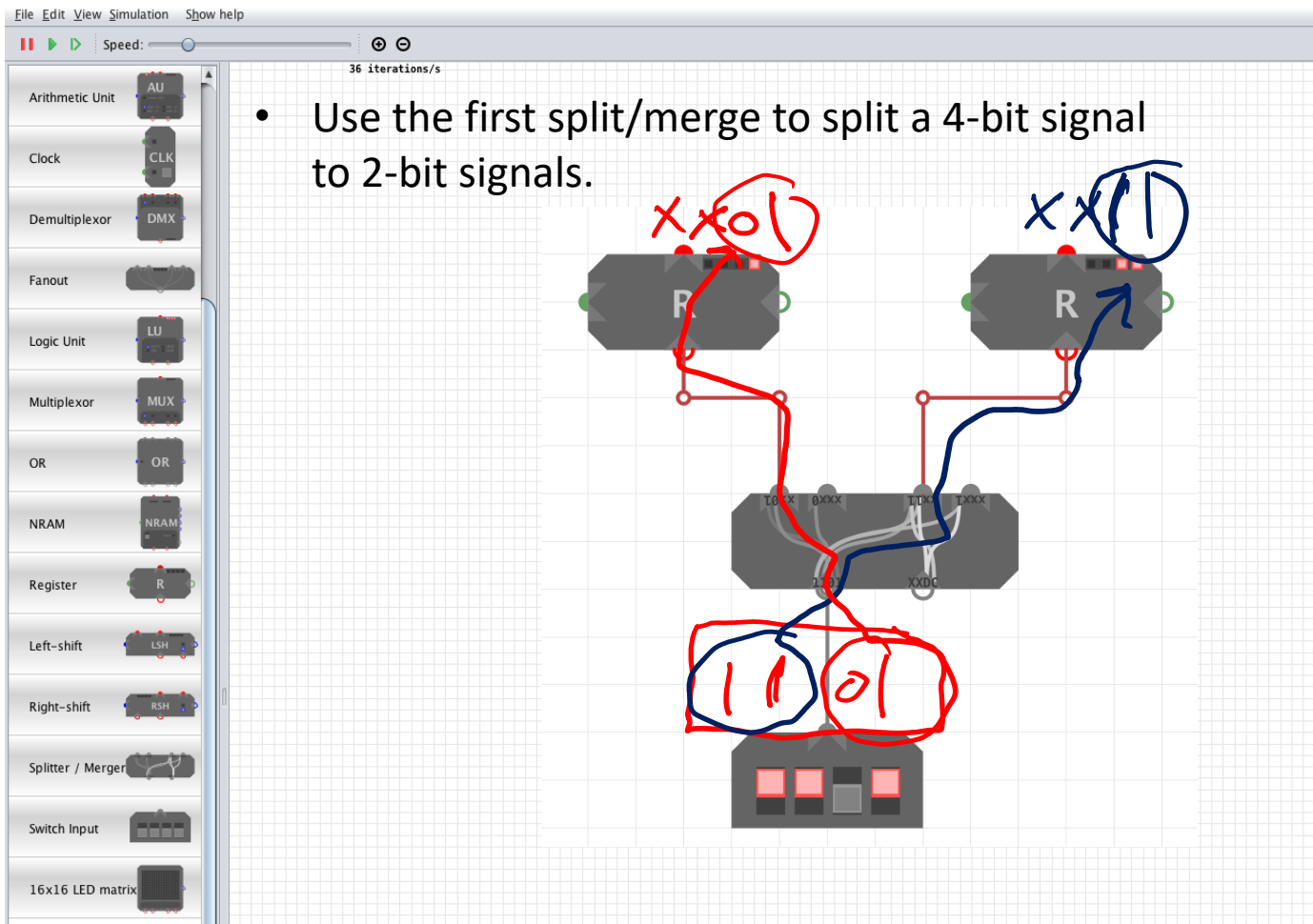

# MUX

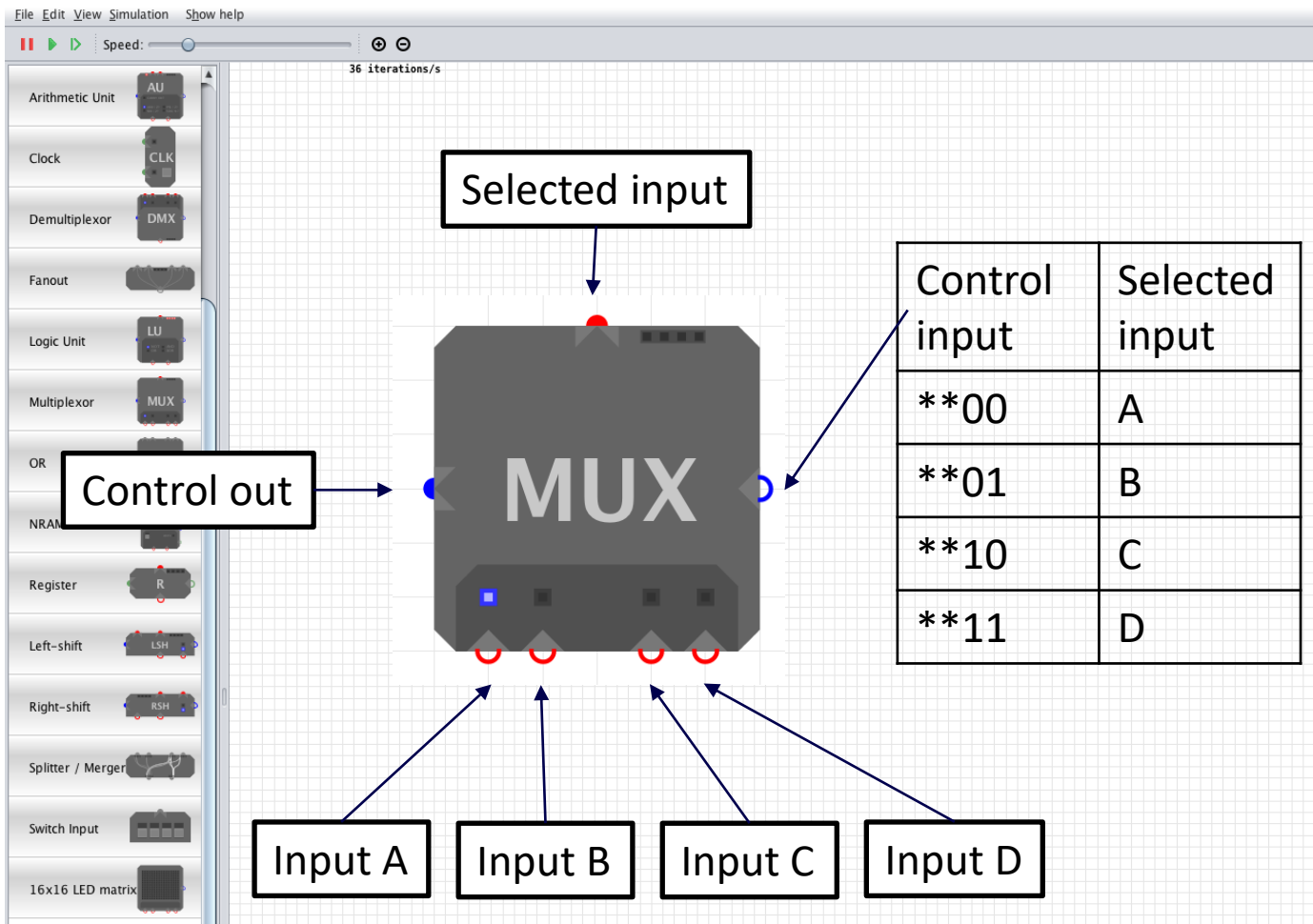

# AND from MUX

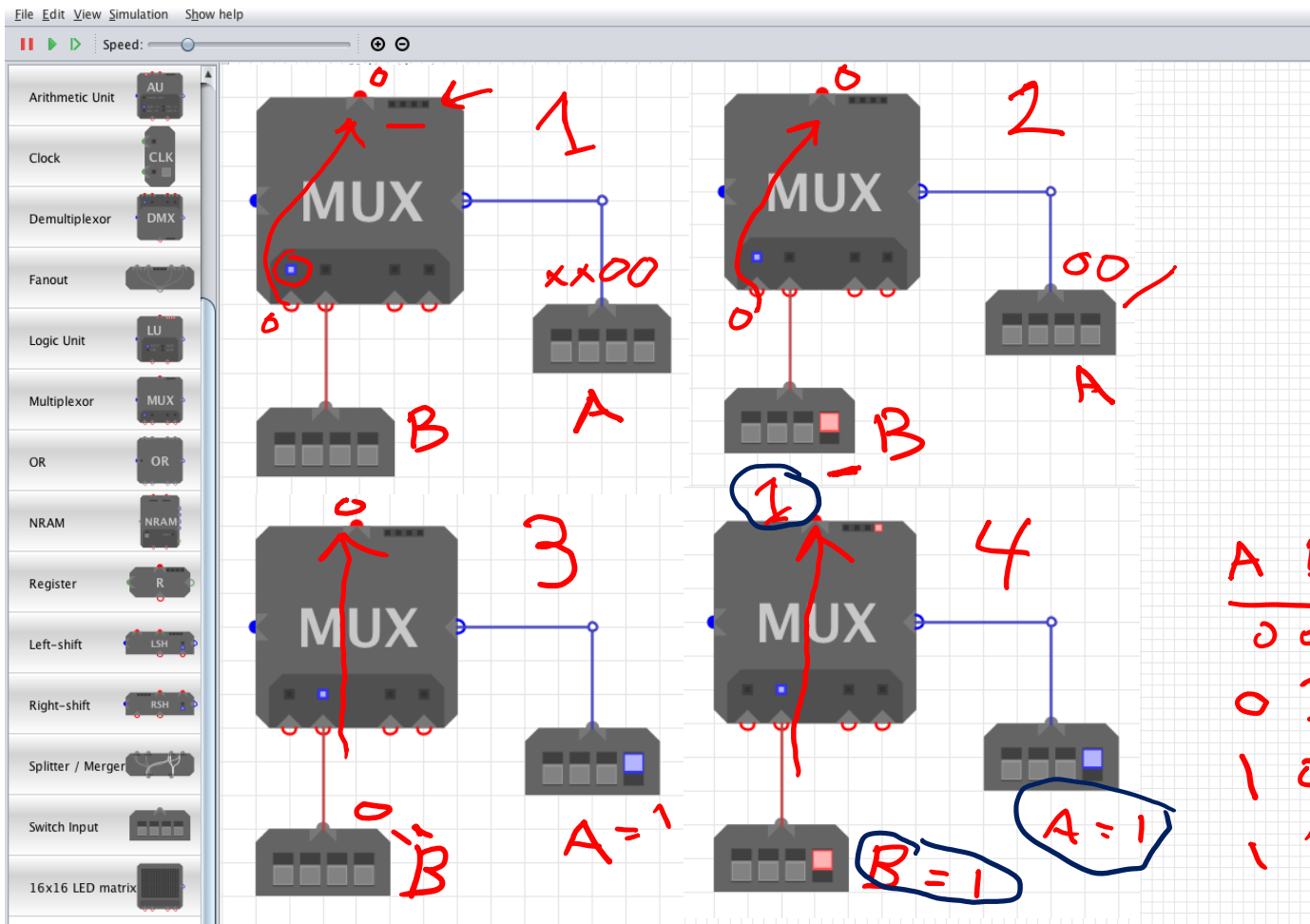


$\begin{matrix} \times \times 0 0 & A \\ \times \times 0 1 & B \\ \times \times 1 0 & C \\ \times \times 1 1 & D \end{matrix}$


A	B	$A \wedge B$
0	0	0
0	1	0
1	0	0
1	1	1





# 🔥 If – Else with MUX

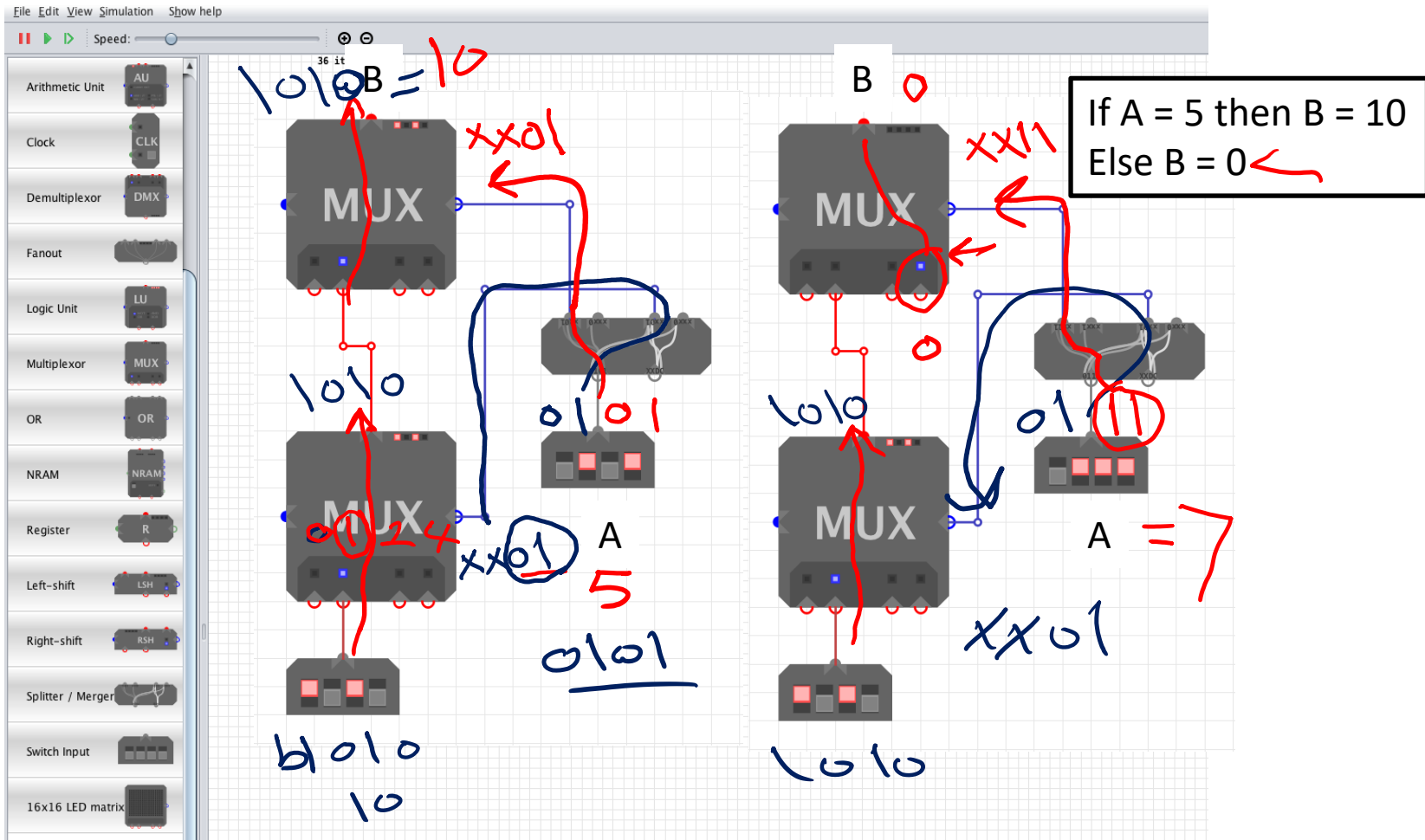

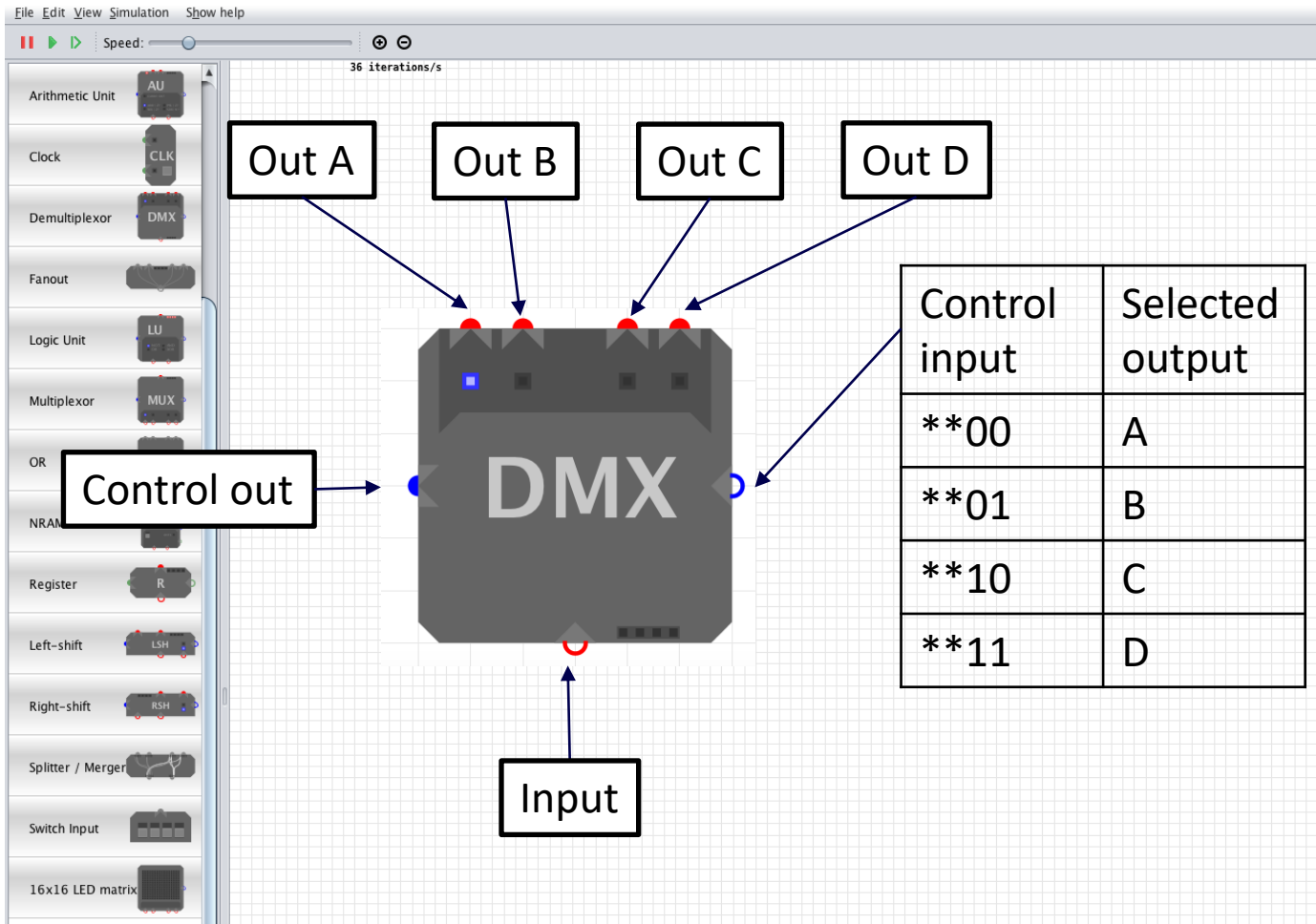


# DMX with counter

File Edit View Simulation Show help  
Speed: 36 iterations/s

- Use a counter and a 2X4 demultiplexer to produce four signals such that one of them is high at a time.

Out1	Out2	Out3	Out4
0001	0000	0000	0000
0000	0001	0000	0000
0000	0000	0001	0000
0000	0000	0000	0001

 - Hint – use the output of the counter to control the demultiplexer.



# 4 X 16 DMX



File Edit View Simulation Show help

Speed: 36 iterations/s

Arithmetic Unit AU

Clock CLK

Demultiplexor DMX

Fanout

Logic Unit LU

Multiplexor MUX

OR

NRAM

Register R

Left-shift LSH

Right-shift RSH

Splitter / Merger

Switch Input


16x16 LED matrix

1. This demultiplexer decodes 2-bit signal into four signals (2 X 4 demux)
2. How many signals can we get be decoding a 4-bit signal?
3. Design a circuit to decode a 4-bit signal using 2X4 demultiplexers.

$2^2 = 4$


$2^4 = 16$

Control input	Selected output
**00	A
**01	B
**10	C
**11	D

 




# Fanout

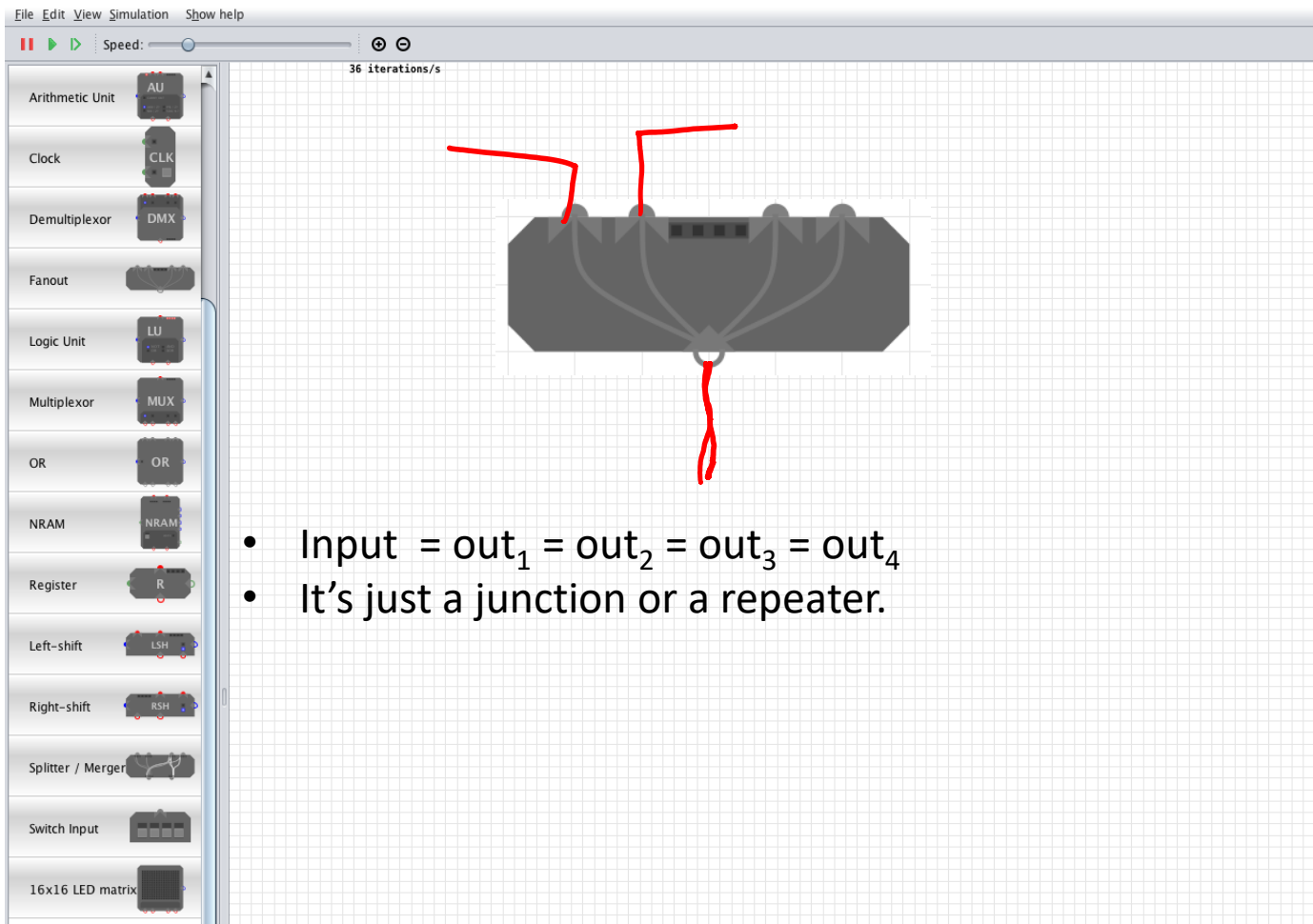

# Memory

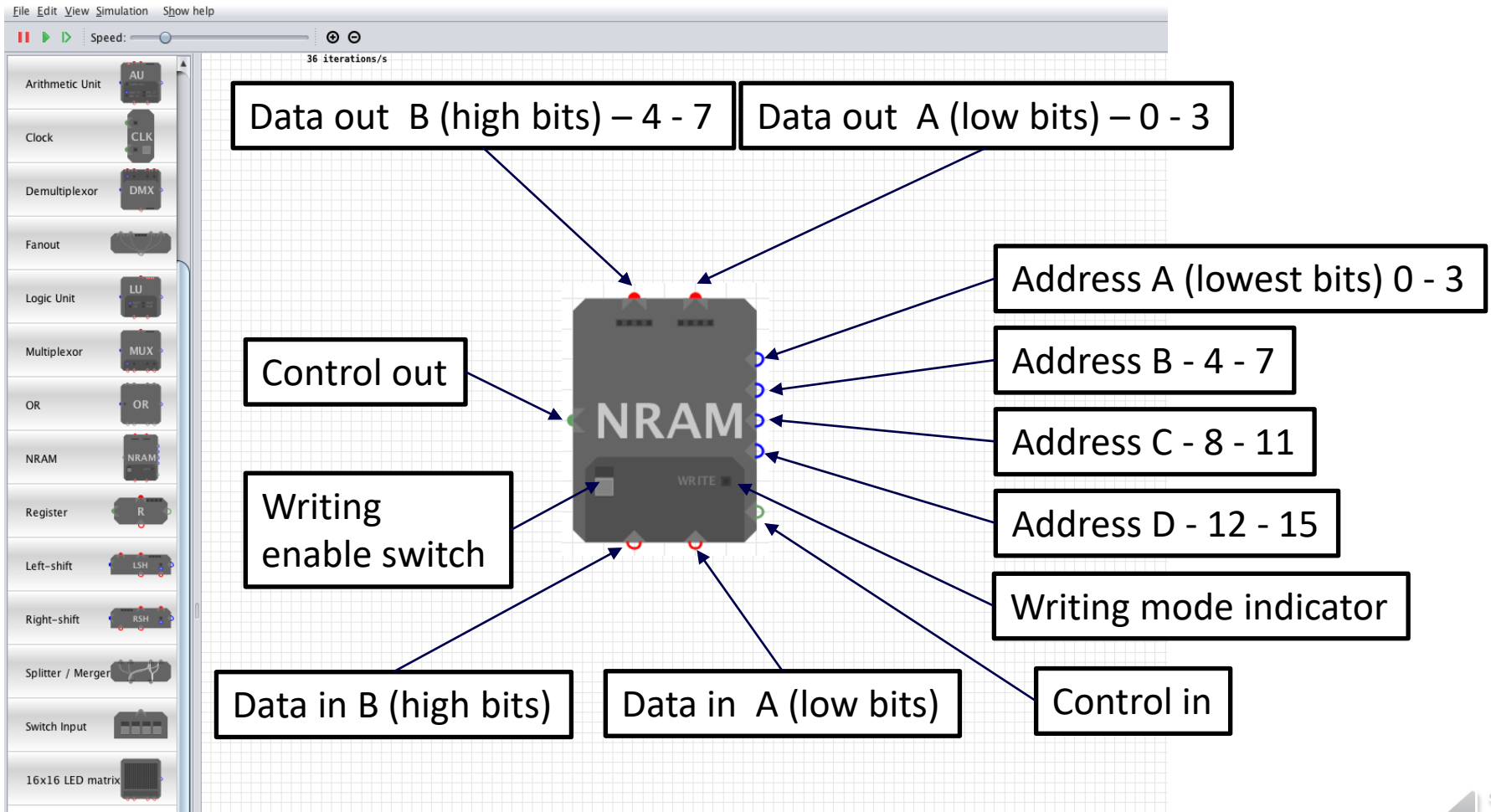

# Memory - size



File Edit View Simulation Show help

Speed: 36 iterations/s

Arithmetic Unit AU

Clock CLK

Demultiplexor DMX

Fanout

Logic Unit LU

Multiplexor MUX

OR

NRAM

Register R

Left-shift LSH

Right-shift RSH

Splitter / Merger

Switch Input

16x16 LED matrix

1. What is the size of the data elements in this memory?
2. How many data elements can we store in this memory?
3. What is the layout of this memory?
4. What is the size of this memory?

data (4 – 7)

data (0 – 3)



Add (0 – 3)

Add (4 – 7)


Add (8 – 11)

Add (12 – 15)






# Memory - read

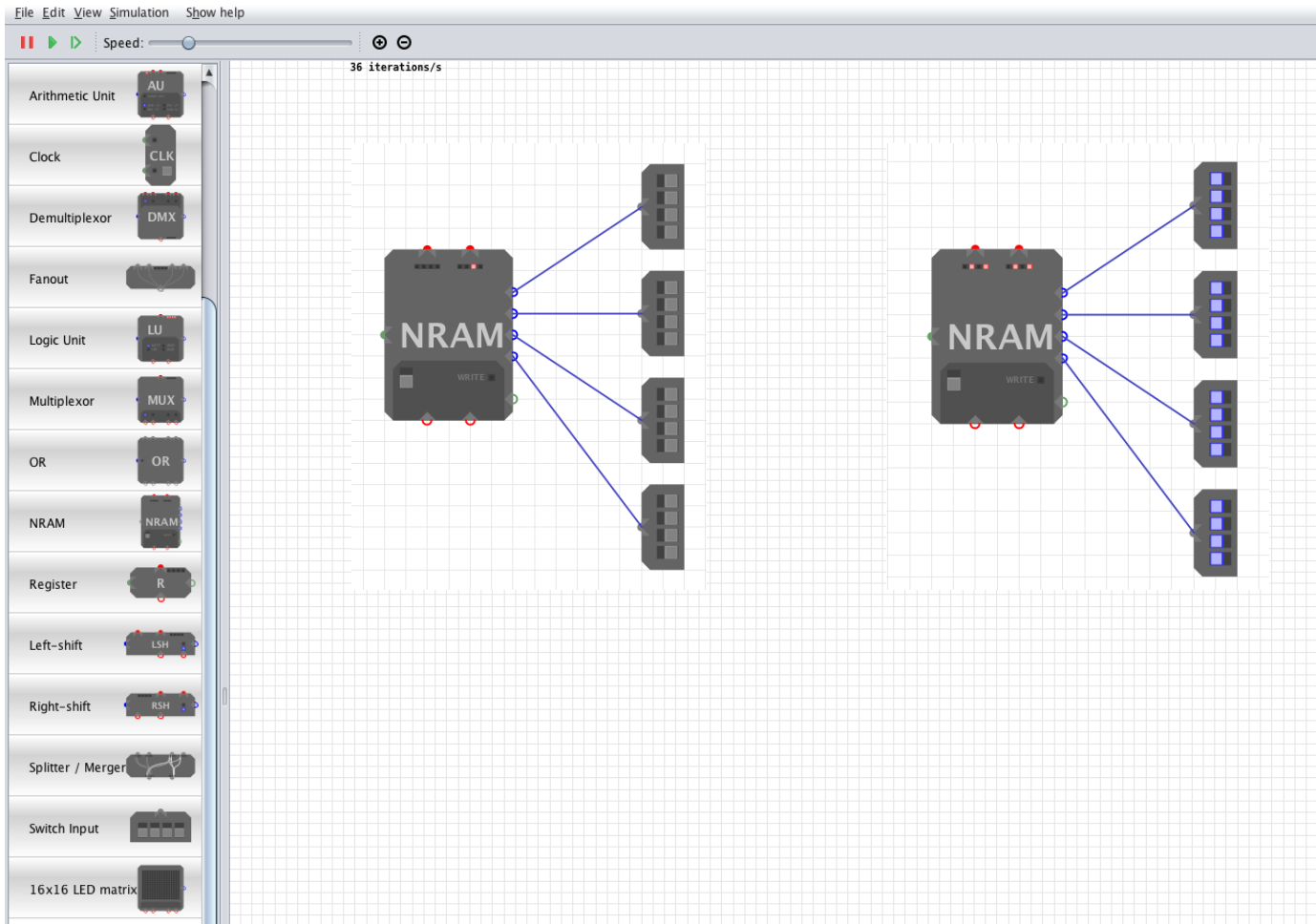

# Memory – write

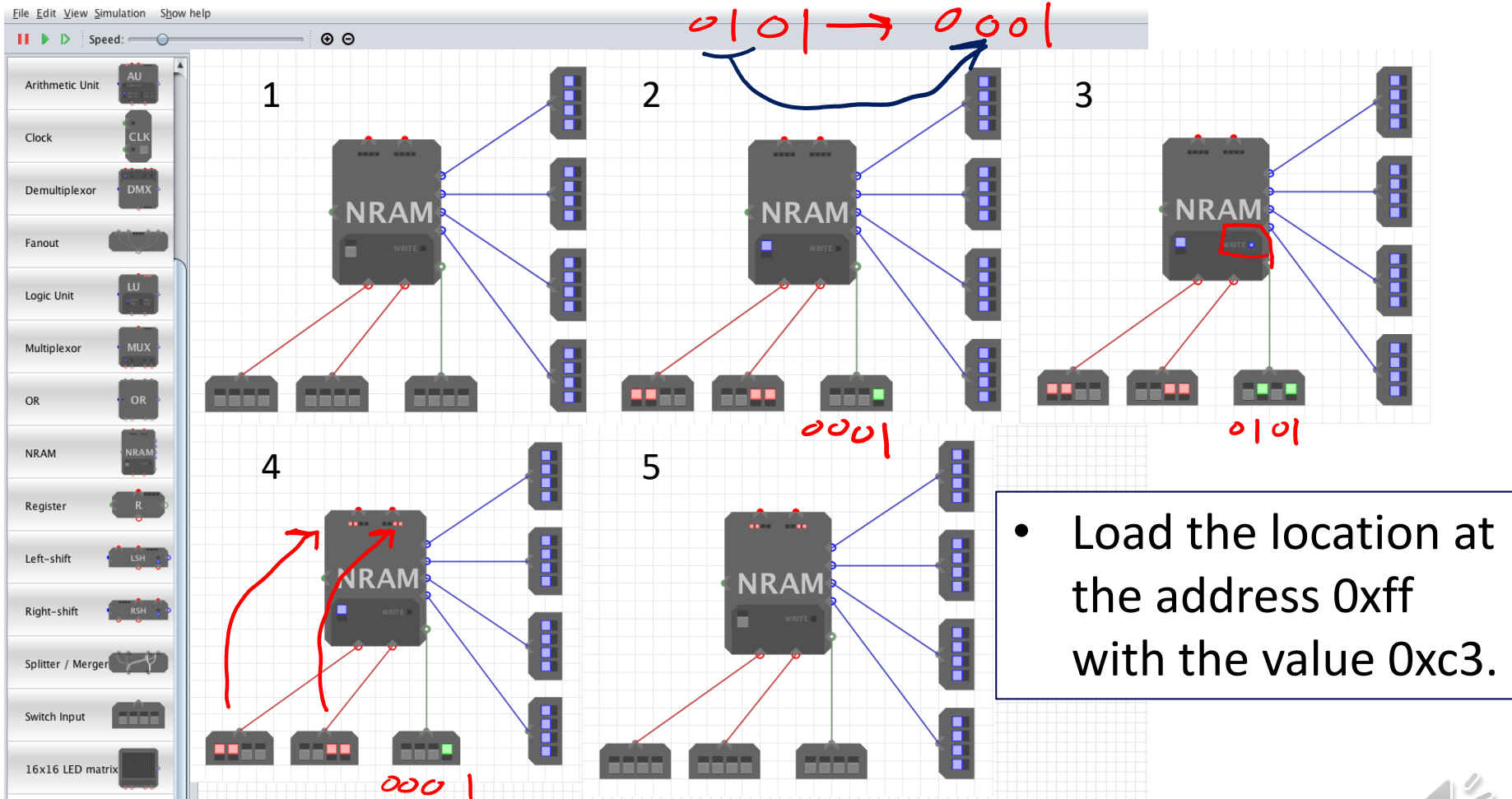

# Memory – load data

The screenshot illustrates the process of loading data into Non-Volatile Random Access Memory (NRAM) within a digital logic simulator. The main workspace shows a circuit with various components like the Arithmetic Unit (AU), Clock (CLK), Demultiplexor (DMX), Fanout, Logic Unit (LU), Multiplexor (MUX), OR gate, NRAM component, Register (R), Left-shift (LSH), Right-shift (RSH), Splitter / Merger, Switch Input, and a 16x16 LED matrix. A context menu is open over the NRAM component, with the option 'View/Edit NRAM Data' highlighted. A separate window titled 'NRAM' displays a table of memory addresses and their corresponding data values. The 'File' menu in this window is open, showing options like 'Load Data', 'Save Data', 'Close without save', and 'Close with save'. A red arrow points to the 'Load Data' option. Below the NRAM window, a 'Data.hex' file is shown, with its contents '02 13 60 48' circled and labeled 'Data.hex'. A red arrow points to this label. The values '02 13 60 48' are also circled in the main workspace, with a red arrow pointing to them from the 'Data.hex' label.

Address	00	01	02	03	04	05
0x000F	00	00	00	00	00	00
0x0014	00	00	00	00	00	00
0x0019	00	00	00	00	00	00
0x001E	00	00	00	00	00	00
0x0023	00	00	00	00	00	00
0x0028	00	00	00	00	00	00
0x002D	00	00	00	00	00	00
0x0032	00	00	00	00	00	00
0x0037	00	00	00	00	00	00
0x003C	00	00	00	00	00	00
0x0041	00	00	00	00	00	00
0x0046	00	00	00	00	00	00
0x004B	00	00	00	00	00	00
0x0050	00	00	00	00	00	00
0x0055	00	00	00	00	00	00
0x005A	00	00	00	00	00	00
0x005F	00	00	00	00	00	00

File menu options:

- Load Data
- Save Data
- Close without save
- Close with save

NRAM data table headers: Go, Last Changed

File menu options: View/Edit NRAM Data, Clear NRAM Data, Add/Edit label, Label size

Data.hex

02 13 60 48


# Memory - design problem -1



File Edit View Simulation Show help  
Speed: 36 iterations/s

- You have two memory components. Design a circuit to copy the content of the first 16 bytes from the first memory to the first 16 bytes of the second memory.

data	address
0x02	0x0
0x13	0x1
0x60	0x2



data	address
0x02	0x0
0x13	0x1
0x60	0x2

# Memory - design problem -2

File Edit View Simulation Show help  
Speed: 36 iterations/s

Arithmetic Unit (AU)  
Clock (CLK)  
Demultiplexor (DMX)  
Fanout  
Logic Unit (LU)  
Multiplexor (MUX)  
OR  
NRAM  
Register (R)  
Left-shift (LSH)  
Right-shift (RSH)  
Splitter / Merger  
Switch Input  
16x16 LED matrix

Extra challenge. Design a circuit to move the data from the first memory to the second memory. The data should be unchanged if the value of each 4bits is greater than zero and to store 0xf for each 4 bits if their value is zero.

data	address
0x02	0x0
0x13	0x1
0x60	0x2

→

data	address
0xf2	0x0
0x13	0x1
0x6f	0x2



# Summary

1. ModuleSim and some of its components.
  1. How clock control registers
  2. How to use Split/Merge
  3. Some applications of multiplexers and demultiplexers.
2. Memory component and two design problem.